


Modules

- The Verilog language describes a digital system as a set of ***modules***.
- Each module has an interface to other modules as well as a description of its contents.
- A module represents a logical unit that can be described either
 - by specifying its internal logical structure — for instance, describing the actual logic gates it is comprised of, or
 - by describing its behavior in a program-like manner — in this case, focusing on what the module does rather than on its logical implementation.
- The modules are then interconnected with nets, allowing them to communicate.

A Structural Description

- A simple NAND latch
 
```
module ffNand;  
    wire    q, qBar;  
    reg     preset, clear;  
  
    nand #1  
        g1 (q, qBar, preset),  
        g2 (qBar, q, clear);  
  
endmodule
```



A Structural Description

- A simple NAND latch

module ffNand; *← Module name*

 wire q, qBar; *← Wire declarations*

 reg preset, clear; *← Register declarations*

 nand #1 *← NAND gate having a delay of one time unit*

 g1 (q, qBar, preset), *← Instantiation of a NAND gate*

 g2 (qBar, q, clear); *← Instantiation of a NAND gate*

endmodule

A Structural Description

- A simple NAND latch
 - Each module definition includes the keyword ***module*** and its name, and is terminated by the ***endmodule*** statement.
 - The wires, declared by the ***wire*** statements, are used to transmit logic values among the submodules of this module.
 - The registers, declared by the ***reg*** statements, represent the storage elements that will hold logic values.
 - NAND gates are one of the predefined logic gate types in the language.
 - The gate instances are connected to the wires and registers.
 - The first label in the parentheses is the gate's output and the others are inputs.

A Structural Description

- Module definition versus module instantiation
 - Using the module statement, we define a module once specifying all of its inner detail.
 - The module may be used (instantiated) in the design many times.
 - Each of these instantiations are called instances of the module, and can be separately named and connected differently.

A Structural Description

- Nets
 - Gates are connected by nets.
 - Nets are one of the two fundamental data types of the language.
 - Registers are the other data type.
 - Nets are used to model an electrical connection between structural entities such as gates.
 - A wire is one type of net.
 - Other net types include wired-AND, wired-OR and trireg connections.
 - The trireg net models a wire as a capacitor that stores electrical charge.
 - Except for the trireg net, nets do not store values but only transmit values that are driven on them.



A Structural Description

- Hierarchical descriptions
 - Several gates or modules are built into larger modules in a hierarchical manner.
 - In a simple NAND latch example, NAND gates were used to build the *ffNand* module.
 - This *ffNand* module could then be used as a piece of a larger module by instantiating it into another module.
 - The use of hierarchical descriptions allows us to control the complexity of a design by breaking the design into smaller and more meaningful submodules.
 - When instantiating the submodules, all we need know about them is their interface.

Simulating a Module

- A simple NAND latch to be simulated

```
module ffNandSim;  
    wire    q, qBar;  
    reg     preset, clear;  
  
    nand #1  
        g1 (q, qBar, preset),  
        g2 (qBar, q, clear);
```


Simulating a Module

initial

begin

\$monitor(\$time,,

“preset = %b clear = %b q = %b qBar = %b”,

preset, clear, q, qBar);

#10 preset = 0; clear = 1;

#10 preset = 1;

#10 clear = 0;

#10 clear = 1;

#10 \$finish;

end

endmodule



Simulating a Module

- A simple NAND latch to be simulated includes
 - A structural description of a simple NAND latch
 - The statements that will provide stimulus to the NAND gate instances
 - The statements that will monitor the changes in the outputs.
- The ***monitor*** statement
 - A simulation command to monitor and print a set of values when any one of the values changes
 - %b represents a printing control for binary.
 - The ,, put extra spaces between the display of the time and the quoted string.

Simulating a Module

- Simulator
 - Executes the statements in the **initial** statement and propagates changed values from the outputs of gates and registers to other gate module inputs.
 - Keeps track of time, causing the changed values appear at some specified time in the future rather than immediately.
 - The future changes are typically stored in a time-ordered event queue.
 - When the simulator has no further statement execution or value propagation to perform at the current time, it finds the next time-ordered event from the event queue, updates time to that of the event, and executes the event.
 - Continues until there are no more events to be simulated or the user halts the simulation.

Simulating a Module

- How does the simulator work in this example ?

- The first assignment statement

`#10 preset = 0; clear = 1;`

specifies the registers *preset* and *clear* will be loaded zero and one respectively 10 time units from the current time (time 0).

- At time 10, *preset* and *clear* are set to zero and one respectively, and then the changed values are propagated.
- At time 11, *q* becomes one, which is the result of *preset* being zero.
- The value of *q* is propagated to the input of NAND gate *g2* which is then scheduled to propagate its changed output 1 time unit in the future.
- At time 12, *qBar* becomes zero.

Simulating a Module

- How does the simulator work in this example ?

- The second assignment statement

`#10 preset = 1;`

specifies the register *preset* will be loaded one 10 time units from the current time (time 10).

- At time 20, *preset* is set to one, and *q* and *qBar* remain constant.

- The third assignment statement

`#10 clear = 0;`

specifies the register *clear* will be loaded zero 10 time units from the current time (time 20).

- At time 30, *clear* is set to zero and the latch changes state after 2 gate delays.

Simulating a Module

- How does the simulator work in this example ?

- The fourth assignment statement

`#10 clear = 1;`

specifies the register *clear* will be loaded one 10 time units from the current time (time 30).

- At time 40, *clear* is set to one, and *q* and *qBar* remain constant.
- The last initial statement

`#10 $finish;`

stops the simulation and returns control to the host operating system at time 50.

Simulating a Module

- Results of simulating the simple NAND latch

0 preset = x clear = x q = x qBar = x

10 preset = 0 clear = 1 q = x qBar = x

11 preset = 0 clear = 1 q = 1 qBar = x

12 preset = 0 clear = 1 q = 1 qBar = 0

20 preset = 1 clear = 1 q = 1 qBar = 0

30 preset = 1 clear = 0 q = 1 qBar = 0


31 preset = 1 clear = 0 q = 1 qBar = 1

32 preset = 1 clear = 0 q = 0 qBar = 1

40 preset = 1 clear = 1 q = 0 qBar = 1

Simulating a Module

 - Results of simulating the simple NAND latch




Simulating a Module

- The four values that a bit may have in the simulator
 - 1 : true (one) state
 - 0 : false (zero) state
 - x : unknown state
 - z : high-impedance state
- Why were *preset* and *clear* defined as registers ?
 - A means of setting and holding the input values during simulation
 - Wires do not hold values but merely transmit values.

Module Hierarchy

- Top-level view

 

Module Hierarchy

- Counter module

```
module m16 (value, clock, fifteen, altFifteen);  
    output [3:0]    value;  
    output          fifteen,  
                  altFifteen;  
    input           clock;
```

Module Hierarchy

```
dEdgeFF a (value[0], clock, ~value[0]),  
        b (value[1], clock, value[1] ^ value[0]),  
        c (value[2], clock, value[2] ^ &value[1:0]),  
        d (value[3], clock, value[3] ^ &value[2:0]);
```

```
assign fifteen = value[0] & value[1] & value[2] & value[3];
```

```
assign altFifteen = &value;
```

```
endmodule
```

Module Hierarchy

- Ports
 - Must be declared to be inputs, outputs, or inout.
- Vectors and scalars
 - The square brackets construct declares the range of bit numbers, the first number being the most significant bit and the second being the least significant bit.
 - The bit numbers used in the specifications must be positive.
 - Registers, nets and ports declared to have a range of bits are said to be vectors.
 - Single-bit registers, nets and ports are said to be scalars.

Module Hierarchy

- Association of ports
 - The order of the names in the instantiation port list must match the order of ports in the definition.
 - Analogous to the software situation where we need to know the order of parameters when calling a subroutine.
 - If the *dEdgeFF* module has the following port definition:

dEdgeFF (q, clock, data)

the instance *a* will have the following connections:

q (output of dEdgeFF)	→ value[0] (output of m16)
clock (input of dEdgeFF)	→ clock (input of m16)
data (input of dEdgeFF)	→ ~value[0] (output of m16)

Module Hierarchy

- Operators used in this example
 - $\sim$: Bitwise negation
Complements each bit in the operand.
 - $\wedge$: Bitwise XOR
Produces the bitwise exclusive OR of two operands.
 - $\&$: Unary reduction AND
Produces the single bit AND of all of the bits of the operand.
 - $\&$: Bitwise AND
Produces the bitwise AND of two operands.
Unary reduction and binary bitwise ANDs are distinguished by syntax.

Module Hierarchy

- The ***assign*** statement
 - Another way of describing a combinational logic function
 - Called continuous assignment statement because the result of the logical expression on the right-hand side of the equal sign is evaluated anytime one of its inputs changes and the result drives the output in a simulation.
 - Allows us to describe a combinational logic function without regard to its actual structural implementation, i.e., there are no instantiated modules.
 - In this example, *fifteen* and *altFifteen* have the same logic function.
- Part-select of a vector
 - A selected range of bits from the entire vector is used in the operation.

value[1:0] ← value[3:0]



Module Hierarchy

- D-type negative edge-triggered flip-flop module

```
module dEdgeFF (q, clock, data);  
    output    q;  
    reg       q;  
    input     clock, data;  
  
    initial  
        #10 q = 0;  
  
    always  
        @(negedge clock) q = #10 data;  
  
endmodule
```

Module Hierarchy

- Registers
 - A register named q drives output q .
 - Register q directly models the flip-flop's storage bit.
 - When simulated, q is initialized to be zero as specified in the initial statement.
- The ***always*** statement
 - Basis for modeling sequential behavior
 - Essentially a while (true) statement
 - Includes one or more procedural statements that are repeatedly executed.
 - The procedural statements within the always statement execute much like a software program.



Module Hierarchy

- `@(negedge clock) q = #10 data;`
 - When there is a negative edge on the *clock* input, then the value of the *data* input will be copied and, after 10 time units, register *q* will be loaded with that copied value.
 - When *q* is loaded, it is loaded with the value that *data* had before the delay started.
- Behavioral descriptions
 - Capture all of the functionality of the module.
 - Leave the actual logical implementation open to the designer.


Module Hierarchy

- Clock generator module

```
module m555 (clock);  
    output    clock;  
    reg       clock;  
  
    initial  
        #5 clock = 1;  
    always  
        #50 clock = ~clock;  
  
endmodule
```

Module Hierarchy

 - Clock generator module
 - The *clock* is initialized to be one after 5 time units have passed.
 - After the first 50 time units have passed, the always statement will be scheduled to execute and change its value.
 - Because *clock* will change value every 50 time units, we have created a clock with a period of 100 time units.



Module Hierarchy

- Two different delay mechanisms

`#50 clock = ~clock;`

`q = #10 data;`

- The first statement waits for 50 time units and loads *clock* with its complement at that time.
- The second statement makes an internal copy of the current value of *data*, waits 10 time units, and then loads *q* with that internal copy.

- The ***timescale*** compiler directive for real time units

``timescale 1ns / 100ps`

- Used to attach units (1ns) and a precision (100ps) for rounding to the time numbers.



Module Hierarchy

- Top-level module

```
module board;
```

```
    wire [3:0]        count;
```

```
    wire              clock, f, af;
```

```
    m16      counter (count, clock, f, af);
```

```
    m555     clockGen (clock);
```

```
    always @(posedge clock)
```


```
        $display ($time,,, "count = %d, f = %d, af = %d", count, f, af);
```

```
endmodule
```



Module Hierarchy

 - Top-level view with internal connections



Module Hierarchy

- The *display* statement
 - Similar to a print statement in a programming language.
 - %d represents a printing control for an unsigned decimal integer.
 - The ,, put extra spaces between the display of the time and the quoted string.
 - In combination with the always statement, the printout in this example will display the values at the positive edge of the *clock*.

Module Hierarchy

- Simulation trace

5 count = x, f = x, af = x

100 count = 1, f = 0, af = 0

200 count = 2, f = 0, af = 0

300 count = 3, f = 0, af = 0

400 count = 4, f = 0, af = 0

500 count = 5, f = 0, af = 0

600 count = 6, f = 0, af = 0

700 count = 7, f = 0, af = 0

800 count = 8, f = 0, af = 0

900 count = 9, f = 0, af = 0



Module Hierarchy

1000 count = 10, f = 0, af = 0

1100 count = 11, f = 0, af = 0

1200 count = 12, f = 0, af = 0

1300 count = 13, f = 0, af = 0

1400 count = 14, f = 0, af = 0

1500 count = 15, f = 1, af = 1

1600 count = 0, f = 0, af = 0

1700 count = 1, f = 0, af = 0

1800 count = 2, f = 0, af = 0

1900 count = 3, f = 0, af = 0



Behavioral Modeling

- Behavioral model
 - An abstraction of how the module works
 - The outputs of the module are described in terms of its inputs.
 - No effort is made to describe how the module is implemented in terms of logic gates.
 - Useful early in the design process, when a designer is more concerned with simulating the system's intended behavior to understand its gross performance characteristics with little regard to its final implementation.
 - Later, structural models with accurate detail of the final implementation are substituted and resimulated to demonstrate functional and timing correctness.

Behavioral Modeling

- Counter module described with behavioral statements

```
module m16Behav (value, clock, fifteen, altFifteen);  
    output [3:0]      value;  
    reg [3:0]         value;  
    output            fifteen, altFifteen;  
    reg               fifteen, altFifteen;  
    input              clock;  
  
    initial  
        value = 0;  
  
    always
```

Behavioral Modeling

```
begin
```

```
    @(negedge clock) #10 value = value + 1;
```

```
    if (value == 15)
```

```
        begin
```

```
            altFifteen = 1; fifteen = 1;
```

```
        end
```

```
    else
```

```
        begin
```

```
            altFifteen = 0; fifteen = 0;
```

```
        end
```

```
    end
```

```
endmodule
```



Behavioral Modeling

- Registers
 - The declaration of the registers and outputs of the same name implicitly connect the outputs of the registers to the ports.
 - In behavioral descriptions, the procedural statements require the use of registers (or variables in software programming) to store the values.
 - The structural version of *m16* did not use registers, rather it implicitly connected the output drivers in the instantiated flip-flops to the output port with a wire.

Behavioral Modeling

- Constant numbers
 - Can be specified in decimal, hexadecimal, octal, or binary.
 - May optionally start with a + or -.
 - Can be given in one of two forms.
 - The first form
 - An unsized decimal number specified using the digits from the sequence 0 to 9
 - Verilog calculates a size for use in an expression.

Behavioral Modeling

- Constant numbers
 - The second form specifies the size of the constant and takes the form:
$$ss...s'fnn...n$$
 - $ss...s$: the size in bits (Specified as a decimal number.)
 - f : the base format (d, h, o, b or D, H, O, B)
 - $nn...n$: the value (For hexadecimal, a ~ f or A ~ F used.)
 - x and z values may be given in all but the decimal base.
 - In hexadecimal, an x or z would represent 4 bits, in octal, 3 bits.
 - Normally, zeros are padded on the left if $nn...n < ss...s$.
 - The first digit of $nn...n$ is x or z, then x or z is padded on the left.
 - An underline character may be inserted to improve readability, which must not be the first character (e.g., 12'b0x0x_1101_0zx1).

Behavioral Modeling

- Constant numbers

- The statement in the example

`altFifteen = 0;`

could be written more exactly as

`altFifteen = 1'b0;`

meaning that one-bit operand with value zero specified in binary is loaded into register *altFifteen*.


- The issue of whether to use one form versus another is a matter of readability and exactness.

Behavioral Modeling

- Mixing structure and behavior
 - The natural evolution of a digital system is from abstract behavior to detailed, implementable structure.
 - Along the design path, the design will be represented at times by a mixture of behavioral and structural models.
 - Not all modules of a design will be designed down to the detailed structural level at the same time.
 - Part of a design may make use of off-the-shelf (pre-designed) hardware.

Fibonacci Number Generator Example

- Top-level view

 

Fibonacci Number Generator Example

- Top-level module

```
module top ();  
    wire                flag, numProduced, numConsumed;  
    wire [15:0]         number, numberOut;  
  
    nandLatch           ready (flag, , numConsumed, numProduced);  
    numberGen           ng (number, numProduced, flag);  
    fibNumberGen        fng (number, flag, numConsumed, numberOut);  
endmodule
```

Fibonacci Number Generator Example

- Operations
 - The seed-number generator module (*ng*) produces a number *n* and passes it onto the Fibonacci number generator module (*fng*).
 - The Fibonacci number generator module (*fng*) calculates the *n*-th Fibonacci number.
 - The latch module (*ready*) is provided for the two modules to signal when to pass another number.
 - The behavioral descriptions in *ng* and *fng* execute concurrently and pass information when the latch output indicates that previous data has been consumed and new valid data is ready.
 - The latch acts as a data-valid signal for a single element queue between producer and consumer modules.

Fibonacci Number Generator Example

- The NAND latch module

```
module nandLatch (q, qBar, set, reset);  
    output    q, qBar;  
    input     set, reset;  
  
    nand #2  
        (q, qBar, set),  
        (qBar, q, reset);  
  
endmodule
```

Fibonacci Number Generator Example

- Instance names
 - Instances of primitive gates, such as NAND and NOR, need not be individually named.
 - Instances of modules must be individually named.

- Unconnected ports

nandLatch ready (flag, , numConsumed, numProduced);



module nandLatch (q, qBar, set, reset);

Fibonacci Number Generator Example

- The seed-number generator module

```
module numberGen (number, numProduced, flag);  
    output [15:0]    number;  
    output          numProduced;  
    input           flag;  
    reg [15:0]      number;  
    reg            numProduced;
```

Fibonacci Number Generator Example

initial

begin

number = 0;

numProduced = 1;

end

always

begin

wait (flag == 1) number = number + 1;

#100 numProduced = 0;

#10 numProduced = 1;

end

endmodule



Fibonacci Number Generator Example

- Operations of the seed-number generator module
 - Waits for the input *flag* to be one.
 - As soon as the input *flag* becomes one, the always statement can then continue executing.
 - The *flag* is the *q* output of the *nandLatch* which, when set, signifies that the previous value has been received and another can be generated.
 - A new seed number is generated when the input *flag* becomes one, and a delay of 100 time units will occur.
 - The *numProduced* is set to zero for 10 time units, causing the *q* output of the *nandLatch* to be cleared to signify that a new number is available.

Fibonacci Number Generator Example

- The Fibonacci number generator module

```
module fibNumberGen (startingValue, flag, numConsumed, fibNum);  
    input [15:0]      startingValue;  
    input            flag;  
    output           numConsumed;  
    output [15:0]     fibNum;  
    reg             numConsumed;  
    reg [15:0]       fibNum;  
    reg [15:0]       count, oldNum, temp;
```

Fibonacci Number Generator Example

initial

begin

numConsumed = 0;

#10 numConsumed = 1;

\$monitor (\$time,, “fibNum = %d, startingValue = %d”,
fibNum, startingValue);

end

always

begin

wait (flag == 0) count = startingValue;

oldNum = 1;



Fibonacci Number Generator Example

```
numConsumed = 0;
#10 numConsumed = 1; // Signal ready for new input data

for (fibNum = 0; count != 0; count = count - 1)
begin
    temp = fibNum;
    fibNum = fibNum + oldNum;
    oldNum = temp;
end
$display ("%d fibNum = %d", $time, fibNum);

end

endmodule
```



Fibonacci Number Generator Example

- Operations of the Fibonacci number generator module
 - Waits for the input *flag* to be zero.
 - The *fibNumberGen* module waits on a signal complementary to what the *numberGen* module waits for.
 - When the input *flag* becomes zero, a 10 time unit pulse is sent out to set the *nandLatch* module and signal the *numberGen* module to begin producing another new seed number.
 - The *n*-th Fibonacci number is calculated in register *fibNum* by the **for** loop statement.
 - The *fibNumberGen* module needs a copy of *startingValue* because it is an input and cannot be changed with a procedural statement.

Fibonacci Number Generator Example

- Edge-triggering versus level-sensitive mechanism
 - The **event control** (@) statement models an edge-triggering mechanism.
$$\text{@(posedge clock) number = number + 1;}$$
 - The **wait** statement is level sensitive.
$$\text{wait (clock == 1) number = number + 1;}$$

Fibonacci Number Generator Example

- Assignment statements
 - The continuous assignment statement

```
wire    a;  
assign  a = b | (c & d);  
or  
wire    a = b | (c & d);
```

- The right-hand side of the equal sign can be thought of as a logic gate whose output is connected to a wire *a*.
- For any change at any time to *b*, *c*, or *d*, the output of the expression will be evaluated and made to drive wire *a*.
- May only drive nets such as a wire.

Fibonacci Number Generator Example

- Assignment statements

- The procedural assignment statement

`oldNum = 1;`

- Found in initial and always statements.
- Can only load values into registers or memory elements.
- The loading of the value is done only when control is transferred to the procedural statement.
- Control is transferred to a procedural assignment statement in a sequential manner, like a normal software program.
- The flow of control is interrupted either by an event (@) or wait statement.

Fibonacci Number Generator Example

- Wires attached to a register

```
reg [15:0]      newValue;
```

```
wire [15:0]     y = newValue;
```

- Wire *y* is connected to the output of register *newValue*.
- Anytime *newValue* is loaded procedurally with a new value, it will drive wire *y* and the inputs it is connected to with that new value.

Testbench

- Testbench approach
 - Better to separate the design's description and the means of testing it.
 - The design may be simulated and monitored through its ports, and later synthesized using other CAD tools such as a logic synthesizer.
 - If the behavior to test a design is included with the design's module, then it should be removed when synthesizing — an error prone process.
 - Testbench approach is to have a top module within which there are two other modules, one representing the system being designed, and the other representing the test generator and monitor.

Testbench

- Top module

```
module testBench;  
    wire      q, qBar, preset, clear;  
  
    design_ffNand    d (q, qBar, preset, clear);  
    test_ffNand      t (q, qBar, preset, clear);  
endmodule
```

Testbench

- Design module

```
module design_ffNand (q, qBar, preset, clear);  
    output    q, qBar;  
    input     preset, clear;  
  
    nand #1  
        g1 (q, qBar, preset),  
        g2 (qBar, q, clear);  
  
endmodule
```

Testbench

- Test module

```
module test_ffNand (q, qBar, preset, clear);  
    input    q, qBar;  
    output   preset, clear;  
    reg      preset, clear;
```

Simulating a Module

```
initial
```

```
begin
```

```
    $monitor($time,,
```

```
        “preset = %b clear = %b q = %b qBar = %b”,
```

```
        preset, clear, q, qBar);
```

```
    #10 preset = 0; clear = 1;
```

```
    #10 preset = 1;
```

```
    #10 clear = 0;
```

```
    #10 clear = 1;
```

```
    #10 $finish;
```

```
end
```

```
endmodule
```

