

Chap 11 : 68 pages

Chap 12 : 49 pages

Chapter #11: Computer Organization

Motivation

- * Computer Design as an application of digital logic design procedure

- * Computer = Processing Unit + Memory System

- * Processing Unit = Control + Datapath

- * Control = Finite State Machine

Inputs = Machine Instruction, Datapath Conditions (**Branch cond.**)

Outputs = Register Transfer Control Signals (**to Datapath, Registers**)

Instruction Interpretation = Instruction Fetch, Decode, Execute

- * Datapath = Functional Units + Registers

Functional Units = ALU, Multipliers, Dividers, etc.

Registers = Program Counter, Shifters, Storage Registers

Chapter Overview

Design of Datapaths and Processor Control Units

* Datapath interconnection strategies:


Point-to-Point, Single Bus, Multiple Busses

• Structure of the State Diagram/ASM Chart to describe controller FSM

ASM (Algorithmic state machine – Program flow chart)

Structure of a Computer

Block Diagram View

 

Structure of a Computer

Example of Instruction Sequencing

Instruction: Add Rx to Ry and place result in Rz

Step 1: *Fetch the (Add instruction) from Memory to Instruction Reg*

Step 2: *Decode Instruction*

Instruction in IR is an ADD

Source operands are Rx, Ry

Destination operand is Rz

(Usually Pipelined)

Step 3: *Execute Instruction*

Move Rx, Ry to ALU

Set up ALU to perform ADD function

ADD Rx to Ry

Move ALU result to Rz

Structure of a Computer

Instruction Types

- * Data Manipulation**

 - Add, Subtract, etc.**

- * Data Staging**

 - Load/Store data to/from memory**

 - Register-to-register move**

- * Control**

 - Conditional/unconditional branches**

 - subroutine call and return**

Structure of a Computer

Control

Elements of the Control Unit (aka Instruction Unit):

Standard FSM things: **(also known as)**

State Register

Next State Logic

Output Logic (datapath control signaling)

Plus Additional "Control" Registers:

Instruction Register (IR)

Program Counter (PC)

Structure of a Computer

Control

Control State Diagram

* Reset

* Fetch Instruction

* Decode


* Execute

Instructions partitioned
into three classes:

* Branch

* Load/Store

* Register-to-Register

 

*Different Sequence
for Each Instruction
Type*

Housekeeping


Structure of a Computer

Datapath

Arithmetic Circuits
constructed in
hierarchical and
iterative fashion

Each bit in datapath
is functionally identical


4-bit
8-bit
16-bit
32-bit
Datapaths

 

**Hierarchical Construction of
Full Adder**

Structure of a Computer

Datapath

 


Bit Slice Concept

iterate to build n-bit wide
datapaths

Datapath

ALU Block Diagram

 

Structure of a Computer

Block Diagram/Register Transfer View


Single Accumulator
Machine

$AC := AC <op> Mem$

"single address
instructions"
AC implicit operand

Arrowed Lines
represent dataflows

others are control flows

 

Memory Address Register
Hold address during memory
accesses

Structure of a Computer

Block Diagram/Register Transfer View

Placement of Data and Instructions in Memory:

- * Data and instructions mixed in memory: Princeton Architecture**
- * Data and instructions in separate memory: Harvard Architecture**

Princeton architecture simpler to implement

Harvard architecture has certain performance advantages:

overlap instruction fetch with operand fetch

We assume the more common Princeton architecture throughout

Structure of a Computer

Block Diagram/Register Transfer View

1. Instruction Fetch:

Move PC to MAR

Initiate a memory read sequence

Move data from memory to IR

2. Instruction Decode:

Op code bits of IR are input to control FSM

Rest of IR bits encode the operand address

Structure of a Computer

Block Diagram/Register Transfer View

3. Operand Fetch:

Move operand address from IR to MAR

Initiate a memory read sequence

4. Instruction Execute:

Data available on load path

Move data to ALU input

Configure ALU to perform ADD operation

Move S result to AC

5. Housekeeping:

Increment PC to point at next instruction

Structure of a Computer

Block Diagram/Register Transfer View

Control: Transfer data from one register to another
Assert appropriate control signals

Register transfer notation

Register to Register moves



Instruction fetch:

PC $\rightarrow$ MAR;
Memory Read;
Memory $\rightarrow$ IR;

-- move PC to MAR
-- assert Memory READ signal
-- load IR from Memory

Instruction Decode: IF IR<op code> = ADD_FROM_MEMORY
THEN

Instruction Execution: IR<addr> $\rightarrow$ MAR;
Memory Read;

-- move operand addr to MAR
-- assert Memory READ signal

*Assert Control
Signal*

Memory $\rightarrow$ ALU B;
AC $\rightarrow$ ALU A;
ALU ADD;

-- gate Memory to ALU B
-- gate AC to ALU A
-- instruct ALU to perform ADD

ALU S $\rightarrow$ AC;

-- gate ALU result to AC

PC+1;

-- increment PC

More Realistic Block Diagram:



Structure of a Computer

Memory Interface

No common clock between CPU and memory

Follow asynchronous 4-cycle handshake request/wait (ack) protocol


In Sequence

1. Request Asserted

2. Wait Unasserted

3. Request Unasserted

4. Wait Asserted

 


Memory cannot make request unless Wait signal is asserted

Hi-to-Lo transition on Wait implies that data is ready (read)
or data has been latched to be sent to memory (write)

Memory Interface

State Diagram Fragments for Read/Write Cycles

 

State 1: drive address bus
assert read request
catch data into MBR

Same behavior on wait
for read and write

State 2: unassert request
hold in state until Wait reasserted

Structure of a Computer

**** I/O Interface**

Memory-Mapped I/O

I/O devices share the memory address space

Control registers manipulated just like memory word

Read/write register to initiate I/O operation

**** 1. Polling**

Programs periodically checks whether I/O has completed

2. Interrupts

Device signals CPU when operation is complete

Software must take over to handle the data transfers from the device

Check for interrupt pending before fetching next instruction

Save PC & vector to special memory location for next instruction

Instruction set includes a "return from interrupt" instruction

Bussing Strategies

Register-to-Register Communications

- * Point-to-point
- * Single shared bus
- * Multiple special purpose busses

Tradeoffs between datapath/control complexity and amount of parallelism supported by the hardware

Case study:

Four general purpose registers that must be able to exchange their contents

Swap instruction must be supported:


SWAP(R_i, R_j)

R_i → R_j;

R_j → R_i;

Bussing Schemes

Point-to-Point Connection Scheme

 

Four registers interconnected via 4:1 Mux's and point-to-point connections

- * Edge-triggered N bit registers controlled by LD_i signals
- * N bit x 4:1 MUXes per register, controlled by S_i<1:0> signals

Bussing Schemes

Point-to-point Connections

Example:

Register transfers $R1 \rightarrow R0$ and $R2 \rightarrow R3$
(can be done simultaneously)


Register transfer operations:

01 $\rightarrow$ S0<1:0>;	Enable path from R1 to R0
10 $\rightarrow$ S3<1:0>;	Enable path from R2 to R3
1 $\rightarrow$ LD0;	Assert load for R0
1 $\rightarrow$ LD3;	Assert load for R3

Bussing Schemes

Point-to-point Connections

 When control signals are asserted and when they take place:



Moore Machine
State Diagram

Enter state X:

Multiplexor control signals asserted
R1 outputs arrive at R0 inputs
R2 outputs arrive at R3 inputs

LD signals asserted

Do not take effect until next rising clock

On entering state Y:


LD signals are synchronous and take
effect at the same time as the state
transition! (Validated with Edge Trigger)

Bussing Schemes

Point-to-point connections

Implementation of Register SWAP operation

SWAP(R1, R2):

 01 → S2<1:0>;		Establish connection paths
10 → S1<1:0>;		
1 → LD2;		Swap takes place at next state transition
1 → LD1;		


Point-to-Point Scheme Plusses and Minuses:

- + transfer a new value into each of the four registers at same time (**Simultaneous transfer possible**)
- + register swap implemented in a single control state

- 5 gates to implement 4:1 MUX
32 bit wide datapath implies 32 x 5 x 4 registers
= 640 gates!
very expensive implementation

Bussing Strategies

Single Bus Interconnection

 

* per register MUX block replaced by single block

* 25% hardware cost of previous alternative

* **shared set of pathways is called a BUS**

Single bus becomes a critical resource --
used by only one transfer at a time

Bussing Strategies

Single Bus Interconnection

Example: R1 → R0 and R2 → R3

State X: (R1 → R0)

01 → S<1:0>;

1 → LD0;

State Y: (R2 → R3)

10 → S<1:0>;

1 → LD3;

Datapath no longer supports two simultaneous transfers!
Thus two control states are required to perform the transfers

Bussing Strategies

Single Bus Interconnection

SWAP Operation

A special TEMP register must be introduced ("Register 4")
MUX's become 5:1 rather than 4:1

State X: (R1 → R4)

001 → S<2:0>;

1 → LD4;

Three states are required rather than one!

plus extra register (R4) and wider mux

State Y: (R2 → R1)

010 → S<2:0>;

1 → LD1;

More control states because this datapath
supports less parallel activity

Engineering choices made based on how
frequently multiple transfers take place at
the same time

State Z: (R4 → R2)


100 → S<2:0>

1 → LD2;

Bussing Strategies

Alternatives to Multiplexors

 Tri-state buffers as an interconnection scheme



Only one register's contents gated to shared bus at a time


Bussing Strategies

Multiple Busses

Real datapaths are a compromise between the two extremes

Register Transfer Diagram

Single Bus Design

 

Register transfer operations: **(all micro-operation listed)**

PC → BUS

IR → BUS

AC → BUS

MBR → BUS

ALU Result → BUS

BUS → PC

BUS → IR

BUS → AC

BUS → MBR

BUS → ALU B

BUS → MAR

AC → ALU A

("hardwired")

Bussing Strategies

Multiple Busses

Example Register Transfer for Single Bus Design

Instruction Interpretation for "ADD Mem[X]"

Fetch Operand

Cycle 1:

IR<operand address> → BUS;
BUS → MAR;

Cycle 2:

Memory Read;
Databus → MBR;

Perform ADD

Cycle 3:

Memory data (MBR) to ALU B

MBR → BUS;
BUS → ALU B;
AC → ALU A;
ADD;

Requires latch
for ALU Result

Write Result


Cycle 4:

ALU Result → BUS;
BUS → AC;

Bussing Strategies

Multiple Busses

 Three Bus Design -- Supports more parallelism



Single bus replaced by three busses:

Memory Bus (MBUS)
Result Bus (RBUS)
Address Bus (ABUS)

Bussing Strategies

Multiple Busses

Instruction Interpretation for "ADD Mem[X]"

Fetch Operand

Cycle 1: IR<operand address> → ABUS;
ABUS → MAR;

Cycle 2: Memory Read;
Databus → MBR;

Perform ADD

Cycle 3: MBR → MBUS;
MBUS → ALU B;
AC → ALU A;
ADD;

Implemented
in three cycles
rather than four
By simultaneous operation

Write Result

ALU Result → RBUS;
RBUS → AC;


**Overlap Cycle 3 + Cycle 4
by separate MBUS and RBUS**

Finite State Machines for Simple CPUs

State Diagram and Datapath Derivation


Processor Specification:

Instruction Format:

 

Load from memory: $\text{Mem}[\text{XXX}] \rightarrow \text{AC};$
 Store to memory: $\text{AC} \rightarrow \text{Mem}[\text{XXX}];$
 Add from memory: $\text{AC} + \text{Mem}[\text{XXX}] \rightarrow \text{AC};$
 Branch if accumulator is negative: $\text{AC} < 0 \Rightarrow \text{XXX} \rightarrow \text{PC};$


Memory Interface:

 

Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

First pass state diagram:

 

Finite State Machines for Simple CPUs


Deriving the State Diagram and Datapath

Assume Synchronous Mealy Machine:

Transitions associated with arcs rather than states

Reset State (State 0)
and Instruction Fetch
Sequence

 On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal



Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Assume Synchronous Mealy Machine:

Transitions associated with arcs rather than states

Reset State (State 0)
and Instruction Fetch
Sequence

On Reset:

zero the PC


Mem Request unasserted

Mem asserts Wait signal

Instruction Fetch:

issue read request

4 cycle handshake on Wait signal

 

Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath


Assume Synchronous Mealy Machine:

Transitions associated with arcs rather than states

Reset State (State 0)
and Instruction Fetch
Sequence

On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal

 Instruction Fetch:
issue read request
4 cycle handshake on Wait signal



Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Assume Synchronous Mealy Machine:


Transitions associated with arcs rather than states

Reset State (State 0)
and Instruction Fetch
Sequence

On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal

Instruction Fetch:
issue read request
4 cycle handshake on Wait signal

 Note: No explicit mention of the
busses being used to implement
register transfers!



Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Assume Synchronous Mealy Machine:


Transitions associated with arcs rather than states

Reset State (State 0)
and Instruction Fetch
Sequence

On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal

Instruction Fetch:
issue read request
4 cycle handshake on Wait signal

 
Note: No explicit mention of the
busses being used to implement
register transfers!



Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Operation Decode State

 

Four Way Next State Branch based on opcode bits


Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

 like IFetch, except that
operand address comes
from IR and data should
be loaded into AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

 like IFetch, except that
operand address comes
from IR and data should
be loaded into AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

 like IFetch, except that
operand address comes
from IR and data should
be loaded into AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath Execution Sequences

Load Sequence

 like IFetch, except that
operand address comes
from IR and data should
be loaded into AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Store Execution Sequence

Memory write sequence

 


Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Store Execution Sequence

Memory write sequence

 


Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Store Execution Sequence

Memory write sequence

 


Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Store Execution Sequence

Memory write sequence

 


Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Add Execution Sequence

 Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Add Execution Sequence

 Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Add Execution Sequence

 Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC




Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath


Add Execution Sequence

 Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC



Finite State Machines for Simple CPUs

 
Deriving the State Diagram and Datapath
Branch Execution Sequence



Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

Branch Execution Sequence

 

Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath


Revised/Complete State Diagram

Simplify Wait Looping

Eliminate some Wait states

At this point, Wait must be asserted, so why loop on $\overline{\text{Wait}}^*$ (same loop condition, both for memory grant)

 Why loop on $\overline{\text{Wait}}$ when resync will take place at state IF0* (same loop condition, both for memory grant)



Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

State Machines Inputs and Outputs so far:

Inputs:


Reset
Wait
IR<15:14>
AC<15>

Outputs:

0 → PC
PC + 1 → PC
PC → MAR
MAR → Memory Address Bus
Memory Data Bus → MBR
MBR → Memory Data Bus
MBR → IR
MBR → AC
AC → MBR
AC + MBR → AC
IR<13:0> → MAR
IR<13:0> → PC
1 → Read/Write
0 → Read/Write
1 → Request

Finite State Machines for Simple CPUs

Processor Signal Flow

 


Finite State Machines for Simple CPUs

Mapping onto Datapath Control

Specification so far is independent of bussing strategy

Implied transfers:

 

This is the point-to-point connection scheme

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

Observe that instruction fetch (**branch, too**) and operand fetch take place at different times

This implies that IR, PC, and MAR transfers can be implemented by single bus (Address Bus)

Combine MBR, IR, ALU B, and AC connections (Memory Bus)


Combine ALU, AC, and MBR connections (Result Bus)

Three bus architecture:

AC + MBR → AC implemented in single state

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

 

AC has two inputs, RBUS and MBUS
(Other registers except MBR have single input and output)

Dual ported configuration is more complex

Better idea: reusing existing paths was possible
MBR → AC transfer implemented by PASS B ALU operation

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

Detailed implementation of register transfer operations

More detailed control operations are called *microoperations*

One register transfer operation = several microoperations

Some operations directly implemented by functional units:


e.g., ADD, Pass B, 0 $\rightarrow$ PC, PC + 1 $\rightarrow$ PC

Some operations require multiple control operations:

e.g., PC $\rightarrow$ MAR implemented as
PC $\rightarrow$ ABUS and ABUS $\rightarrow$ MAR (**micro-operation**)

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

 


Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

Timing of State Changes and Microoperations

Consider Edge
Triggered Register

 

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

Relationship between register transfer and microoperations:

<u>Register Transfer</u>	<u>Microoperations</u>
0 → PC	0 → PC (delayed);
PC + 1 → PC	PC + 1 → PC (delayed);
PC → MAR	PC → ABUS (immediate), ABUS → MAR (delayed);
MAR → Address Bus	MAR → Address Bus (immediate);
Data Bus → MBR	Data Bus → MBR (delayed);
MBR → Data Bus	MBR → Data Bus (immediate);
MBR → IR	MBR → ABUS (immediate), ABUS → IR (delayed);
MBR → AC	MBR → MBUS (immediate), MBUS → ALU B (immediate), ALU PASS B (immediate), ALU Result → RBUS (immediate), RBUS → AC (delayed);

Register Transfer : Delayed
Register → Bus : Immediate
Bus → Register : Delayed
(remember Edge Triggered)

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

Relationship between register transfer and microoperations:

Register Transfer

Microoperations

AC → MBR

AC → RBUS (immediate),

RBUS → MBR (delayed);

AC + MBR → AC

AC → ALU A (immediate),

MBR → MBUS (immediate),

MBUS → ALU B (immediate),

ALU ADD (immediate),

ALU Result → RBUS (immediate),

RBUS → AC (delayed);

IR<13:0> → MAR

IR → ABUS (immediate),

ABUS → IR (delayed);

IR<13:0> → PC

IR → ABUS (immediate),

ABUS → PC (delayed);

1 → Read/Write

Read (immediate);

0 → Read/Write

Write (immediate);

1 → Request


Request (immediate);

**Special microoperations for AC → ALU and ALU Result → RBUS
not strictly necessary since these connections can be hardwired**

Finite State Machines for Simple CPUs

Mapping onto Datapath Operations

Revised microoperation signal flow

 

4 inputs

make sure that Reset and Wait are synchronized

16 datapath control lines

2 memory control lines

Controller Implementation

Chapter Summary

- * *Basic organization of the Von Neumann computer*

Separation of processor and memory

- * *Datapath connectivity*

- * *Control Unit Organization*

Register transfer operation