

Introduction to CMOS VLSI Design

Lecture 10: Sequential Circuits

Outline

- ☐ Floorplanning
- ☐ Sequencing
- ☐ Sequencing Element Design
- ☐ Max and Min-Delay
- ☐ Clock Skew
- ☐ Time Borrowing
- ☐ Two-Phase Clocking


Project Strategy

- ❑ Proposal
 - Specifies inputs, outputs, relation between them
 - ❑ Floorplan
 - Begins with block diagram
 - Annotate dimensions and location of each block
To supply with critical or explanatory notes
 - Requires detailed paper design
 - ❑ Schematic
 - Make paper design simulate correctly
 - ❑ Layout
 - Physical design, DRC, NCC, ERC
- Network Consistency Checking
LVS" (Layout vs. Schematic)
- Electrical Rule Check
(This command examines the
current facet and checks
all well areas for proper electrical
rules)
- Design Rule Check

Floorplan

- ❑ How do you estimate block areas?
 - Begin with block diagram
 - Each block has
 - Inputs
 - Outputs
 - Function (draw schematic)
 - Type: array, datapath, random logic
- ❑ Estimation depends on type of logic


MIPS Floorplan

 

Area Estimation

- ❑ Arrays:
 - Layout basic cell (first step)
 - Calculate core area from # of cells
 - Allow area for decoders, column circuitry
- ❑ Datapaths
 - Sketch slice plan
 - Count area of cells from cell library
 - Ensure wiring is possible
- ❑ Random logic
 - Compare complexity do a design you have done

MIPS Slice Plan

 


Typical Layout Densities

- ❑ Typical numbers of high-quality layout
- ❑ Derate by 2 for class projects to allow routing and some sloppy layout.
- ❑ Allocate space for big wiring channels


Element	Area
Random logic (2 metal layers)	1000-1500 λ^2 / transistor
Datapath	250 – 750 λ^2 / transistor Or 6 WL + 360 λ^2 / transistor
SRAM	1000 λ^2 / bit
DRAM	100 λ^2 / bit
ROM	100 λ^2 / bit

Sequencing

 - ❑ *Combinational logic*
 - output depends on current inputs
- ❑ *Sequential logic*
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called *state* or *tokens*
 - Ex: FSM, pipeline



Finite State Machine

 

Pipeline

Dispersion is a phenomenon that causes the separation of a wave into spectral components with different wavelengths, due to a dependence of the wave's speed on its wavelength

Sequencing Cont.


- ❑ If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- ❑ Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But *dispersion* sets min time between pulses
- ❑ This is called *wave pipelining* in circuits
- ❑ In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.

Sequencing Overhead

- ❑ Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- ❑ Inevitably adds some delay to the slow tokens
- ❑ Makes circuit slower than just the logic delay
 - Called sequencing overhead (need margin for latch, FF)
- ❑ Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence


Sequencing Elements

 - ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger



Sequencing Elements

 - ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger



Latch Design

- ☐ Pass Transistor Latch

- ☐ Pros

 - +

 - +

- ☐ Cons

 -


 -

 -

 -

 -

 -

 

Latch Design

- ❑ Pass Transistor Latch

- ❑ Pros

 - + Tiny

 - + Low clock load

- ❑ Cons

 - V_t drop


 - nonrestoring

 - backdriving

 - output noise sensitivity

 - dynamic

 - diffusion input

 


Used in 1970's

Latch Design

□ Transmission gate


+

-

 

Latch Design

 - ❑ Transmission gate
 - + No V_t drop
 - Requires inverted clock



Latch Design

❑ Inverting buffer

+


+

+ Fixes either

•


•

—

 

Latch Design

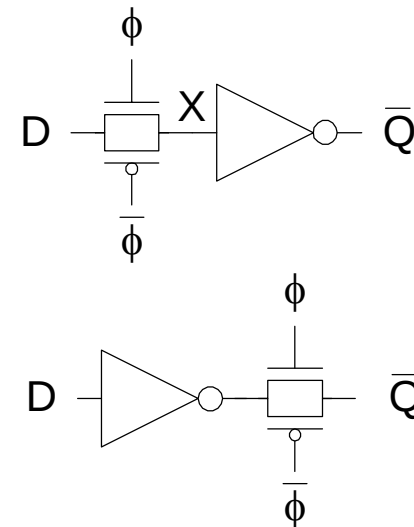- ❑ Inverting buffer
 - + Restoring
 - + No backdriving
 - + Fixes either
 - Output noise sensitivity
 - Or diffusion input
 - Inverted output




Latch Design

❑ Tristate feedback


+

—

 

Latch Design

 - ❑ Tristate feedback
 - + Static
 - Backdriving risk
- ❑ Static latches are now essential




Latch Design

□ Buffered input


+

+

 


Latch Design

 - ❑ Buffered input
 - + Fixes diffusion input
 - + Noninverting




☐ Buffered output
+

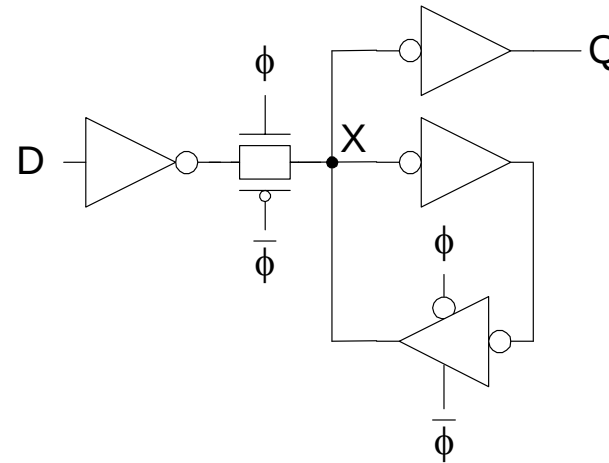

Latch Design

- ❑ Buffered output
+ No backdriving

 


- ❑ Widely used in standard cells
 - + Very robust (most important)
 - Rather large
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading

Latch Design

□ Datapath latch


+

-

 


Latch Design

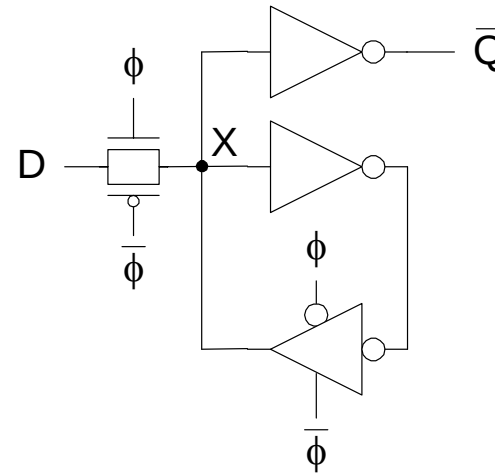- ❑ Datapath latch
 - + Smaller, faster
 - unbuffered input




Flip-Flop Design

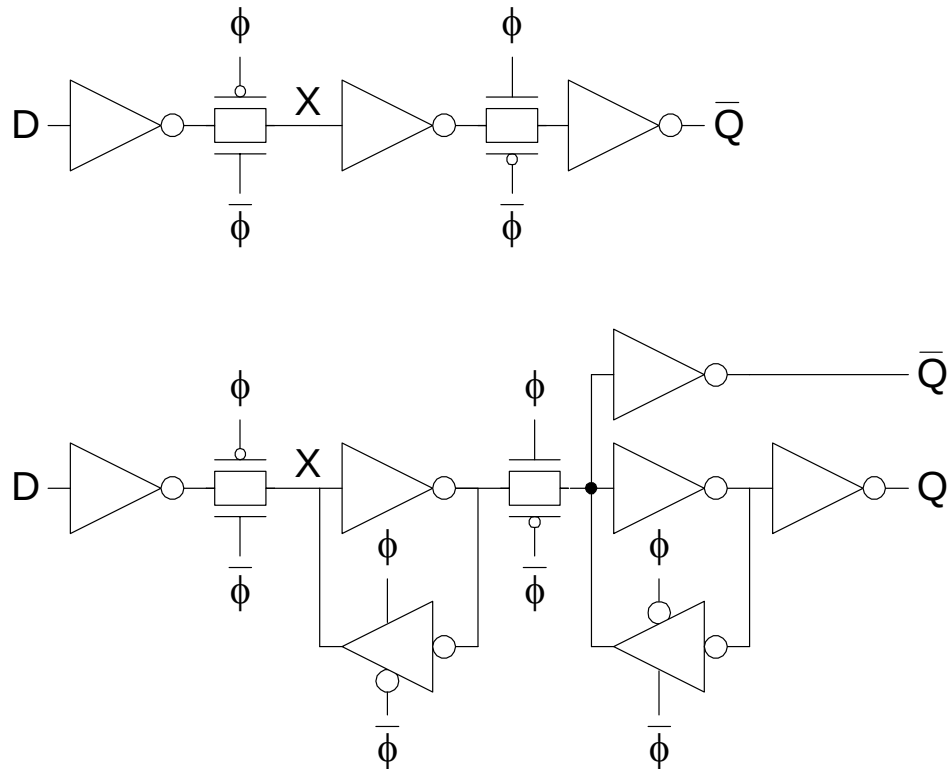- ❑ Flip-flop is built as pair of back-to-back latches




Enable

 - ❑ Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew




Reset

 - ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous




Set / Reset

 - ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset



Sequencing Methods






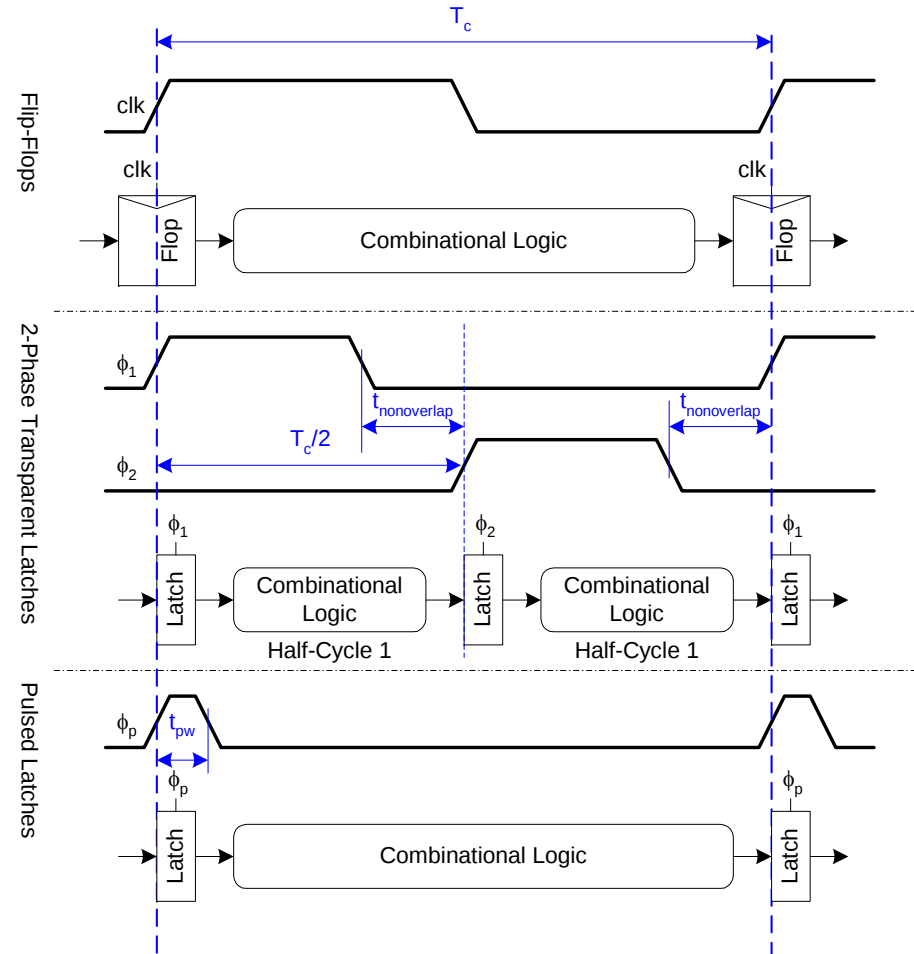
- ❑ Flip-flops
- ❑ 2-Phase Latches
- ❑ Pulsed Latches




Timing Diagrams

Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk-Q Prop Delay
t_{cca}	Latch/Flop Clk-Q Cont. Delay
t_{pdq}	Latch D-Q Prop Delay
t_{pcq}	Latch D-Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

  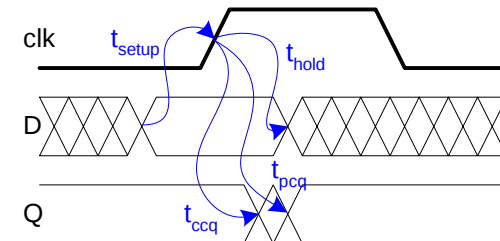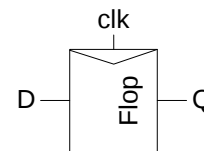  


Max-Delay: Flip-Flops

 


Max-Delay: Flip-Flops
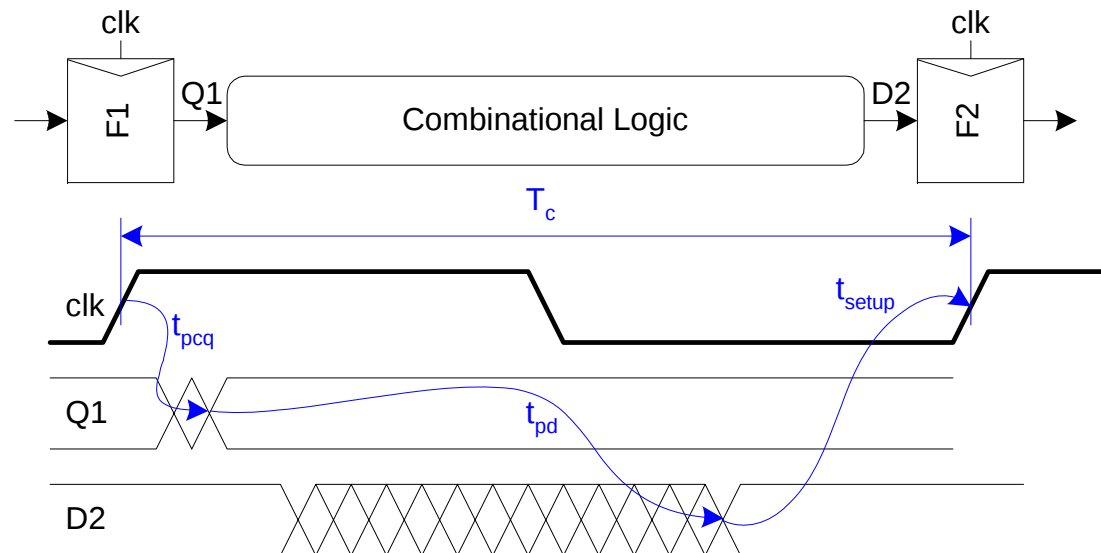
$$t_{pd} \leq T_c - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$



Max Delay: 2-Phase Latches

 
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{\hspace{2cm}}_{\text{sequencing overhead}}$$



Max Delay: 2-Phase Latches

$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

 
Latch (Transparent)
used
so set up time
disregarded



(skip)

Max Delay: Pulsed Latches
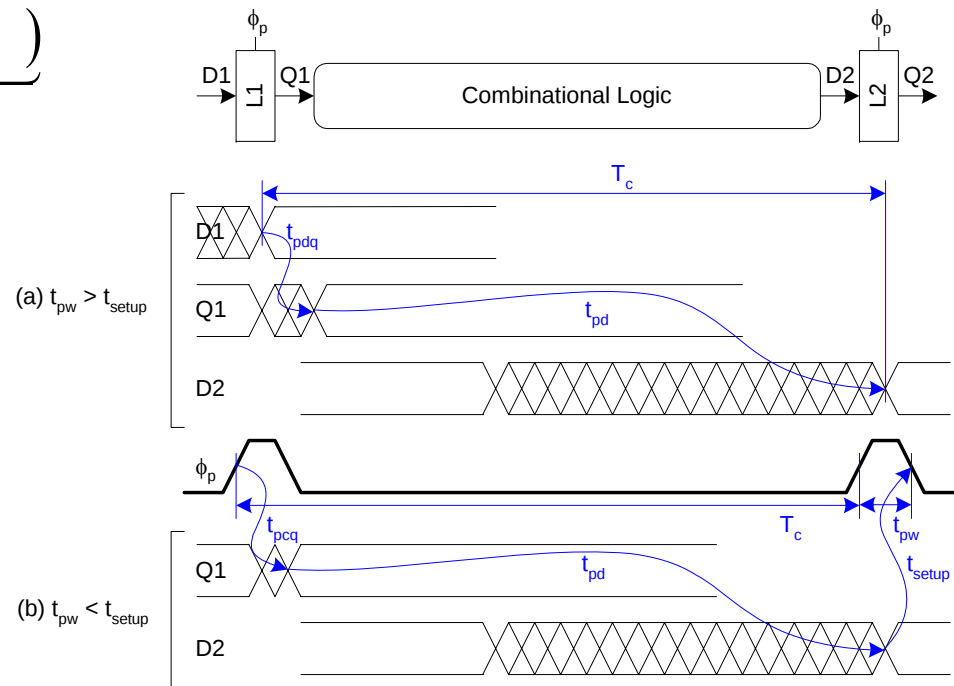
$$t_{pd} \leq T_c - \underbrace{\max(\quad)}_{\text{sequencing overhead}}$$




(skip)

Max Delay: Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}}$$


Data driven

Clock driven

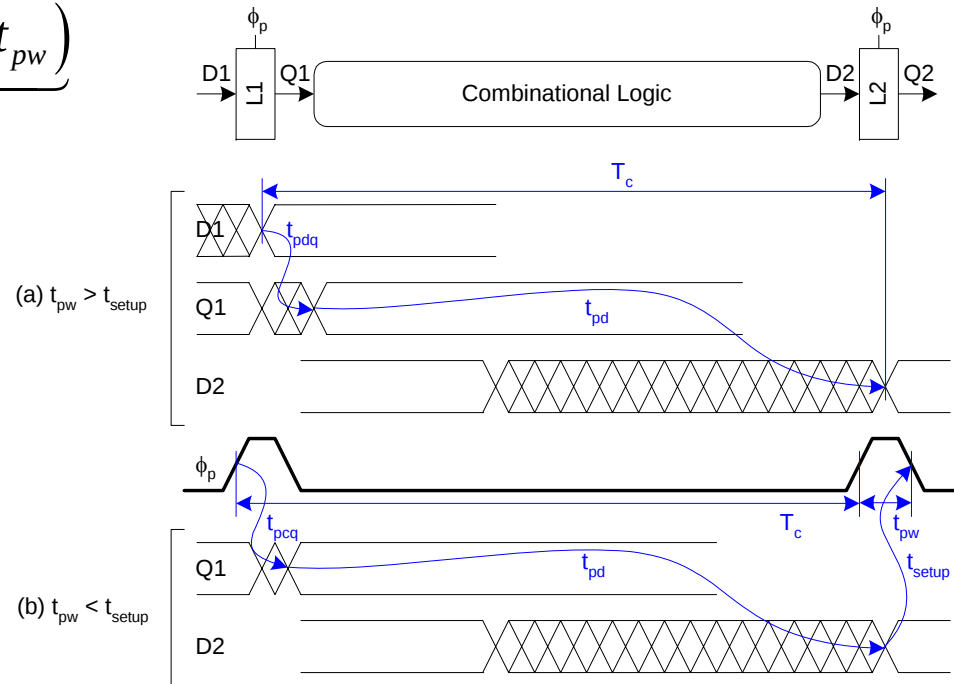

Min-Delay: Flip-Flops

$$t_{cd} \geq$$

 


Min-Delay: Flip-Flops

Logic contamination delay

$$t_{cd} \geq t_{hold} - t_{ccq}$$

 t_{hold} is min value so t_{cd}
should be larger than the right side




Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.

But a flop is made of two latches!

 

Min-Delay: 2-Phase Latches


$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.

But a flop is made of two latches!

→ Two phase or single phase

 


(skip)

Min-Delay: Pulsed Latches

$$t_{cd} \geq$$

Hold time increased
by pulse width

 


(skip)

Min-Delay: Pulsed Latches

$$t_{cd} \geq t_{\text{hold}} - t_{ccq} + t_{pw}$$


Hold time increased
by pulse width

 

Time Borrowing

- ❑ In a flop-based system:
 - Data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
 - Flops have hard edges
- ❑ In a latch-based system
 - Data can pass through latch while transparent
 - Long cycle of logic can borrow time into next
 - As long as each loop completes in one cycle

Time Borrowing Example

 


How Much Borrowing?

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches
 
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$





Clock Skew

- ❑ We have assumed zero clock skew
- ❑ Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
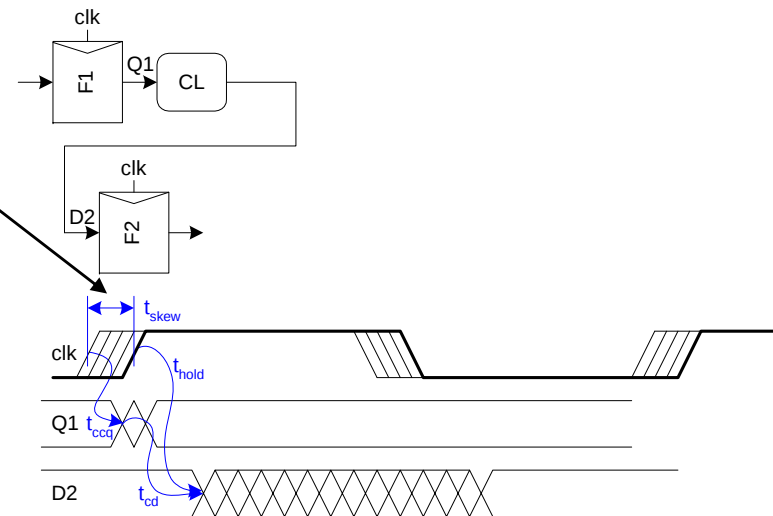 
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$



Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$

Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$
 
$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$




Two-Phase Clocking

- ❑ If setup times are violated, reduce clock speed
- ❑ If hold times are violated, chip fails at any speed
- ❑ In this class, working chips are most important
 - No tools to analyze clock skew
- ❑ An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- ❑ Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop

- ❑ In class, use flip-flop with nonoverlapping clocks
 - Very slow – nonoverlap adds to setup time
 - But no hold times

 (See pp.48)
- ❑ In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk



Summary

- ❑ Flip-Flops:
 - Very easy to use, supported by all tools
- ❑ 2-Phase Transparent Latches:
 - Lots of skew tolerance and time borrowing
- ❑ Pulsed Latches:
 - Fast, some skew tol & borrow, hold time risk

	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay t_{cd}	Time borrowing t_{borrow}
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\tau} + t_{skew})$	$t_{hold} - t_{ccq} + t_{p\tau} + t_{skew}$	$t_{p\tau} - (t_{setup} + t_{skew})$