

Introduction to CMOS VLSI Design

Lecture 19: Design for Skew

Outline

- ☐ Clock Distribution
- ☐ Clock Skew
- ☐ Skew-Tolerant Static Circuits
- ☐ Traditional Domino Circuits
- ☐ Skew-Tolerant Domino Circuits

Clocking


- ❑ Synchronous systems use a clock to keep operations in sequence
 - Distinguish *this* from *previous* or *next*
 - Determine speed at which machine operates
- ❑ Clock must be distributed to all the sequencing elements
 - Flip-flops and latches
- ❑ Also distribute clock to other elements
 - Domino circuits and memories

Clock Distribution

- ❑ On a small chip, the clock distribution network is just a wire
 - And possibly an inverter for clk_b
- ❑ On practical chips, the RC delay of the wire resistance and gate load is very long
 - Variations in this delay cause clock to get to different elements at different times
 - This is called *clock skew*
- ❑ Most chips use repeaters to buffer the clock and equalize the delay
 - Reduces but doesn't eliminate skew

 Example

- ❑ Skew comes from differences in gate and wire delay
 - With right buffer sizing, clk_1 and clk_2 could ideally arrive at the same time.
 - But power supply noise changes buffer delays
 - clk_2 and clk_3 will always see RC skew




Review: Skew Impact

- ❑ Ideally full cycle is available for work
- ❑ Skew adds sequencing overhead
- ❑ Increases hold time too





$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
 
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$



Cycle Time Trends

    - ❑ Much of CPU performance comes from higher f
 - f is improving faster than simple process shrinks
 - Sequencing overhead is bigger part of cycle



Solutions

- ❑ Reduce clock skew
 - Careful clock distribution network design
 - Plenty of metal wiring resources
- ❑ Analyze clock skew
 - Only budget actual, not worst case skews
 - Local vs. global skew budgets
- ❑ Tolerate clock skew
 - Choose circuit structures insensitive to skew

Clock Dist. Networks


- ☐ *Ad hoc*
- ☐ Grids
- ☐ H-tree
- ☐ Hybrid

Clock Grids


- ❑ Use grid on two or more levels to carry clock
- ❑ Make wires wide to reduce RC delay
- ❑ Ensures low skew between nearby points
- ❑ But possibly large skew across die

Alpha Clock Grids





Alpha 21064

 


Alpha 21164

 


Alpha 21264

    

Alpha 21064

 


Alpha 21164

 

Alpha 21264


H-Trees

 - ❑ Fractal structure
 - Gets clock arbitrarily close to any point
 - Matched delay along all paths
- ❑ Delay variations cause skew
- ❑ A and B might see big skew



Itanium 2 H-Tree

 - ❑ Four levels of buffering:
 - Primary driver
 - Repeater
 - Second-level clock buffer
 - Gater
- ❑ Route around obstructions



Hybrid Networks

- ❑ Use H-tree to distribute clock to many points
- ❑ Tie these points together with a grid

- ❑ Ex: IBM Power4, PowerPC
 - H-tree drives 16-64 sector buffers
 - Buffers drive total of 1024 points
 - All points shorted together with grid

Skew Tolerance

- ❑ Flip-flops are sensitive to skew because of *hard edges*
 - Data launches at latest rising edge of clock
 - Must setup before earliest next rising edge of clock
 - Overhead would shrink if we can soften edge
- ❑ Latches tolerate moderate amounts of skew
 - Data can arrive anytime latch is transparent

Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$

Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$


$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$
 
$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$




Dynamic Circuit Review

 - ❑ Static circuits are slow because fat pMOS load input
- ❑ Dynamic gates use precharge to remove pMOS transistors from the inputs
 - Precharge: $\phi = 0$ output forced high
 - Evaluate: $\phi = 1$ output may pull low



Domino Circuits

 - ❑ Dynamic inputs must monotonically rise during evaluation
 - Place inverting stage between each dynamic gate
 - Dynamic / static pair called domino gate
- ❑ Domino gates can be safely cascaded




Domino Timing

- ❑ Domino gates are 1.5 – 2x faster than static CMOS
 - Lower logical effort because of reduced C_{in}
- ❑ Challenge is to keep precharge off critical path
- ❑ Look at clocking schemes for precharge and eval
 - Traditional schemes have severe overhead
 - Skew-tolerant domino hides this overhead

Traditional Domino Ckts

- ❑ Hide precharge time by ping-ponging between half-cycles
 - One evaluates while other precharges
 - Latches hold results during precharge


$$t_{pd} = T_c - 2t_{pdq}$$

 

Clock Skew


- ❑ Skew increases sequencing overhead
 - Traditional domino has hard edges
 - Evaluate at latest rising edge
 - Setup at latch by earliest falling edge
 
$$t_{pd} = T_c - 2t_{\text{setup}} - 2t_{\text{skew}}$$



Time Borrowing

 - ❑ Logic may not exactly fit half-cycle
 - No flexibility to borrow time to balance logic between half cycles
- ❑ Traditional domino sequencing overhead is about 25% of cycle time in fast systems!




Relaxing the Timing

- ❑ Sequencing overhead caused by hard edges
 - Data departs dynamic gate on late rising edge
 - Must setup at latch on early falling edge
- ❑ Latch functions
 - Prevent glitches on inputs of domino gates
 - Holds results during precharge
- ❑ Is the latch really necessary?
 - No glitches if inputs come from other domino
 - Can we hold the results in another way?


Skew-Tolerant Domino

 - ❑ Use overlapping clocks to eliminate latches at phase boundaries.
 - Second phase evaluates using results of first



Full Keeper

 
- ❑ After second phase evaluates, first phase precharges
- ❑ Input to second phase falls
 - Violates monotonicity?
- ❑ But we no longer need the value
- ❑ Now the second gate has a floating output
 - Need full keeper to hold it either high or low



Time Borrowing


- ❑ Overlap can be used to
 - Tolerate clock skew
 - Permit time borrowing
- ❑ No sequencing overhead

$$t_{pd} = T_c$$

 


Multiple Phases

 - ❑ With more clock phases, each phase overlaps more
 - Permits more skew tolerance and time borrowing



Clock Generation

 

Summary

- ❑ Clock skew effectively increases setup and hold times in systems with hard edges
- ❑ Managing skew
 - Reduce: good clock distribution network
 - Analyze: local vs. global skew
 - Tolerate: use systems with soft edges
- ❑ Flip-flops and traditional domino are costly
- ❑ Latches and skew-tolerant domino perform at full speed even with moderate clock skews.