

Introduction to CMOS VLSI Design

Lecture 3: CMOS Transistor Theory

Outline

- ☐ Introduction
- ☐ MOS Capacitor
- ☐ nMOS I-V Characteristics
- ☐ pMOS I-V Characteristics
- ☐ Gate and Diffusion Capacitance
- ☐ Pass Transistors
- ☐ RC Delay Models


Introduction

- ❑ So far, we have treated transistors as ideal switches
- ❑ An ON transistor passes a finite amount of current
 - Depends on terminal voltages
 - Derive current-voltage (I-V) relationships
- ❑ Transistor gate, source, drain all have capacitance
 - $I = C (\Delta V / \Delta t) \rightarrow \Delta t = (C / I) \Delta V$
 - Capacitance and current determine speed
- ❑ Also explore what a “degraded level” really means




MOS Capacitor

 - ❑ Gate and body form MOS capacitor
- ❑ Operating modes
 - Accumulation
 - Depletion
 - Inversion




Terminal Voltages

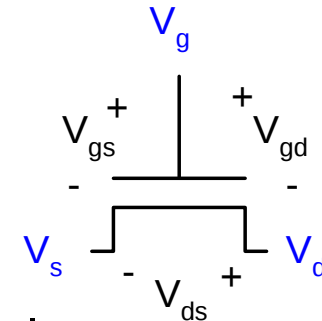- ❑ Mode of operation depends on V_g , V_d , V_s
 - $V_{gs} = V_g - V_s$
 - $V_{gd} = V_g - V_d$
 - $V_{ds} = V_d - V_s = V_{gs} - V_{gd}$
- ❑ Source and drain are symmetric diffusion terminals
 - By convention, source is terminal at lower voltage
 - Hence $V_{ds} \geq 0$
- ❑ nMOS body is grounded. First assume source is 0 too.
- ❑ Three regions of operation
 - *Cutoff*
 - *Linear*
 - *Saturation*




nMOS Cutoff

- ❑ No channel
- ❑ $I_{ds} = 0$

 


nMOS Linear

 - ❑ Channel forms
- ❑ Current flows from d to s
 - e^- from s to d
- ❑ I_{ds} increases with V_{ds}
- ❑ Similar to linear resistor



nMOS Saturation

 - ❑ Channel pinches off
- ❑ I_{ds} independent of V_{ds}
- ❑ We say current saturates
- ❑ Similar to current source




I-V Characteristics

- ❑ In Linear region, I_{ds} depends on
 - How much charge is in the channel?
 - How fast is the charge moving?



Channel Charge

 - ❑ MOS structure looks like parallel plate capacitor while operating in inversion
 - Gate – oxide – channel
- ❑ $Q_{\text{channel}} =$



Channel Charge

 
 
- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
 - Gate – oxide – channel
- ❑ $Q_{\text{channel}} = CV$
- ❑ $C =$



Channel Charge

- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
 - Gate – oxide – channel
- ❑ $Q_{\text{channel}} = CV$
- ❑ $C = C_g = \epsilon_{\text{ox}} WL / t_{\text{ox}} = C_{\text{ox}} WL$
- ❑ $V =$

 
 
$$C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$$



Channel Charge

- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
 - Gate – oxide – channel
- ❑ $Q_{\text{channel}} = CV$
- ❑ $C = C_g = \epsilon_{\text{ox}} WL / t_{\text{ox}} = C_{\text{ox}} WL$
- ❑ $V = V_{\text{gc}} - V_t = (V_{\text{gs}} - V_{\text{ds}}/2) - V_t$
  
$$C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$$



Carrier velocity

- ❑ Charge is carried by e-
- ❑ Carrier velocity v proportional to lateral E-field between source and drain
- ❑ $v =$

Carrier velocity

- ❑ Charge is carried by e-
- ❑ Carrier velocity v proportional to lateral E-field between source and drain
- ❑ $v = \mu E$ μ called mobility
- ❑ $E =$

Carrier velocity

- ❑ Charge is carried by e-
- ❑ Carrier velocity v proportional to lateral E-field between source and drain
- ❑ $v = \mu E$ μ called mobility
- ❑ $E = V_{ds}/L$
- ❑ Time for carrier to cross channel:
 - $t =$

Carrier velocity

- ❑ Charge is carried by e-
- ❑ Carrier velocity v proportional to lateral E-field between source and drain
- ❑ $v = \mu E$ μ called mobility
- ❑ $E = V_{ds}/L$
- ❑ Time for carrier to cross channel:
 - $t = L / v$

nMOS Linear I-V

□ Now we know

- How much charge Q_{channel} is in the channel
- How much time t each carrier takes to cross

$$I_{ds} =$$

nMOS Linear I-V

□ Now we know

- How much charge Q_{channel} is in the channel
- How much time t each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$
$$=$$

nMOS Linear I-V

□ Now we know

- How much charge Q_{channel} is in the channel
- How much time t each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$\beta = \mu C_{\text{ox}} \frac{W}{L}$$

nMOS Saturation I-V

- ❑ If $V_{gd} < V_t$, channel pinches off near drain
 - When $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current

$$I_{ds} =$$

nMOS Saturation I-V

- ❑ If $V_{gd} < V_t$, channel pinches off near drain
 - When $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current

$$I_{ds} = \beta \left(V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat}$$

nMOS Saturation I-V

- ❑ If $V_{gd} < V_t$, channel pinches off near drain
 - When $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current

$$\begin{aligned} I_{ds} &= \beta \left(V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat} \\ &= \frac{\beta}{2} (V_{gs} - V_t)^2 \end{aligned}$$


nMOS I-V Summary

□ Shockley 1st order transistor models

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

 Example

- ❑ We will be using a 0.6 μm process for your project
 - From AMI Semiconductor
 - $t_{\text{ox}} = 100 \text{ \AA}$
 - $\mu = 350 \text{ cm}^2/\text{V}\cdot\text{s}$
 - $V_t = 0.7 \text{ V}$
- ❑ Plot I_{ds} vs. V_{ds}
 - $V_{\text{gs}} = 0, 1, 2, 3, 4, 5$
 - Use $W/L = 4/2 \lambda$



$$\beta = \mu C_{\text{ox}} \frac{W}{L} = (350) \left(\frac{3.9 \cdot 8.85 \cdot 10^{-14}}{100 \cdot 10^{-8}} \right) \left(\frac{W}{L} \right) = 120 \frac{W}{L} \mu\text{A}/\text{V}^2$$

pMOS I-V


- ❑ All dopings and voltages are inverted for pMOS
- ❑ Mobility μ_p is determined by holes
 - Typically 2-3x lower than that of electrons μ_n
 - 120 cm²/V*s in AMI 0.6 μ m process
- ❑ Thus pMOS must be wider to provide same current
 - In this class, assume $\mu_n / \mu_p = 2$
 - *** plot I-V here

Capacitance

- ❑ Any two conductors separated by an insulator have capacitance
- ❑ Gate to channel capacitor is very important
 - Creates channel charge necessary for operation
- ❑ Source and drain have capacitance to body
 - Across reverse-biased diodes
 - Called diffusion capacitance because it is associated with source/drain diffusion


Gate Capacitance

 - Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox} WL / t_{ox} = C_{ox} WL = C_{permicron} W$
- $C_{permicron}$ is typically about 2 fF/ μm




Diffusion Capacitance

 - ❑ C_{sb} , C_{db}
- ❑ Undesirable, called *parasitic* capacitance
- ❑ Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_g for contacted diff
 - $\frac{1}{2} C_g$ for uncontacted
 - Varies with process




Pass Transistors

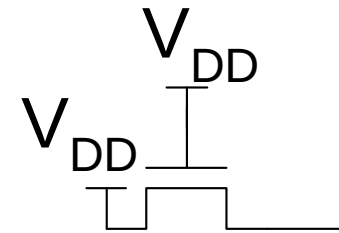- ❑ We have assumed source is grounded
- ❑ What if source > 0 ?
 - e.g. pass transistor passing V_{DD}







Pass Transistors




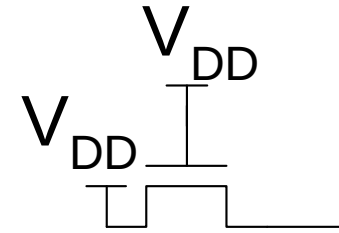
- ❑ We have assumed source is grounded
- ❑ What if source > 0 ?
 - e.g. pass transistor passing V_{DD}
- ❑ $V_g = V_{DD}$
 - If $V_s > V_{DD} - V_t$, $V_{gs} < V_t$
 - Hence transistor would turn itself off
- ❑ nMOS pass transistors pull no higher than $V_{DD} - V_{tn}$
 - Called a degraded “1”
 - Approach degraded value slowly (low I_{ds})
- ❑ pMOS pass transistors pull no lower than V_{tp}



Pass Transistor Ckts

    

Pass Transistor Ckts

 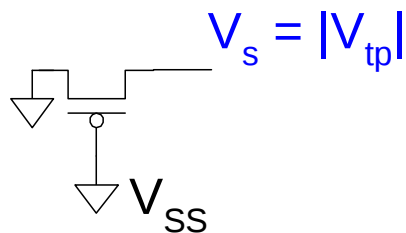 
 


Effective Resistance

- ❑ Shockley models have limited value
 - Not accurate enough for modern transistors
 - Too complicated for much hand analysis
- ❑ Simplification: treat transistor as resistor
 - Replace $I_{ds}(V_{ds}, V_{gs})$ with effective resistance R
 - $I_{ds} = V_{ds}/R$
 - R averaged across switching of digital gate
- ❑ Too inaccurate to predict current at any given time
 - But good enough to predict RC delay

RC Delay Model

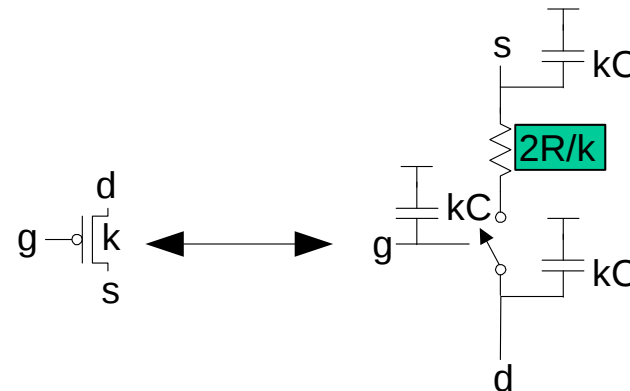 - ❑ Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- ❑ Capacitance proportional to width
- ❑ Resistance inversely proportional to width



RC Values

❑ Capacitance

- $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width
- Values similar across many processes

❑ Resistance


- $R \approx 6 \text{ K}\Omega \cdot \mu\text{m}$ in $0.6\mu\text{m}$ process (Sheet R을 사용할 것)
- Improves with shorter channel lengths

❑ Unit transistors

- May refer to minimum contacted device ($4/2 \lambda$)
- Or maybe $1 \mu\text{m}$ wide device
- Doesn't matter as long as you are consistent


Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter




Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter




Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter



Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter



$$d = 6RC$$