

---

# Logical Effort

(Sizing, Staging, Fan out)

# Design for Performance

---

## □ Reduce $C_L$

- internal diffusion capacitance of the gate itself
  - keep the drain diffusion as small as possible
- interconnect capacitance
- fanout

## □ Increase $W/L$ ratio of the transistor

- the most powerful and effective performance optimization tool in the hands of the designer
- watch out for **self-loading!** – when the intrinsic capacitance dominates the extrinsic load

## □ Increase $V_{DD}$

- can trade-off energy for performance
- increasing  $V_{DD}$  above a certain level yields only very minimal improvements
- reliability concerns enforce a firm upper bound on  $V_{DD}$

# NMOS/PMOS Ratio

---


- ❑ So far have sized the PMOS and NMOS so that the  $R_{eq}$ 's match (ratio of 3 to 3.5)
  - symmetrical VTC
  - equal high-to-low and low-to-high propagation delays
  
- ❑ If speed is the only concern, **reduce** the width of the PMOS device!
  - widening the PMOS degrades the  $t_{pHL}$  due to larger parasitic capacitance

$$\beta = (W/L_p)/(W/L_n)$$

$r = R_{eqp}/R_{eqn}$  (resistance ratio of identically-sized PMOS and NMOS)

$$\beta_{opt} = \sqrt{r} \text{ when wiring capacitance is negligible}$$

# PMOS/NMOS Ratio Effects

 

$\beta$  of 2.4 (= 31 k $\Omega$ /13 k $\Omega$ ) gives symmetrical response

$\beta$  of 1.6 to 1.9 gives optimal performance

# Device Sizing for Performance

---

□ Divide capacitive load,  $C_L$ , into

- $C_{int}$  : intrinsic - diffusion and Miller effect
- $C_{ext}$  : extrinsic - wiring and fanout

$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$$


- where  $t_{p0} = 0.69 R_{eq} C_{int}$  is the intrinsic (**unloaded**) delay of the gate

□ Widening both PMOS and NMOS by a factor **S** reduces  $R_{eq}$  by an identical factor ( $R_{eq} = R_{ref}/S$ ), but raises the **intrinsic** capacitance by the same factor ( $C_{int} = SC_{iref}$ )

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref})) = t_{p0} (1 + C_{ext}/(SC_{iref}))$$

- $t_{p0}$  is independent of the sizing of the gate; *with no load the drive of the gate is totally offset by the increased capacitance*
- any  $S$  sufficiently larger than  $(C_{ext}/C_{int})$  yields the best performance gains with least area impact

# Sizing Impacts on Delay

 

The majority of the improvement is already obtained for  $S = 5$ . Sizing factors larger than 10 barely yield any extra gain (and cost significantly more area).

self-loading effect  
(intrinsic capacitance dominates)

## Impact of Fanout on Delay

---

- Extrinsic capacitance,  $C_{\text{ext}}$ , is a function of the fanout of the gate - the larger the fanout, the larger the external load.
- First determine the **input loading** effect of the inverter. Both  $C_g$  and  $C_{\text{int}}$  are proportional to the gate sizing, so  $C_{\text{int}} = \gamma C_g$  is independent of gate sizing and


$$t_p = t_{p0} (1 + C_{\text{ext}} / \gamma C_g) = t_{p0} (1 + f/\gamma)$$

i.e., the delay of an inverter is a function of the ratio between its external load capacitance and its input gate capacitance: the **effective fan-out**  $f$

$$f = C_{\text{ext}} / C_g$$
 
# Inverter Chain

- Real goal is to minimize the delay through an inverter chain



the delay of the j-th inverter stage is

$$t_{p,j} = t_{p0} (1 + C_{g,j+1}/(\gamma C_{g,j})) = t_{p0}(1 + f_j/\gamma)$$

and 
$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

so 
$$t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1}/(\gamma C_{g,j}))$$

- If  $C_L$  is given
  - How should the inverters be sized?
  - How many stages are needed to minimize the delay?



## Sizing the Inverters in the Chain

- The optimum size of each inverter is the geometric mean of its neighbors – meaning that if each inverter is sized up by the same factor  $f$  wrt the preceding gate, it will have the same effective fan-out and the same delay

$$f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$$


where  $F$  represents the overall effective fan-out of the circuit ( $F = C_L/C_{g,1}$ )

and the minimum delay through the inverter chain is

$$t_p = N t_{p0} (1 + (\sqrt[N]{F}) / \gamma)$$

- The relationship between  $t_p$  and  $F$  is linear for one inverter, square root for two, etc.

## Example of Inverter Chain Sizing

 


- $C_L/C_{g,1}$  has to be evenly distributed over  $N = 3$  inverters

$$C_L/C_{g,1} = 8/1$$

$$f =$$

## Example of Inverter Chain Sizing

 

- $C_L/C_{g,1}$  has to be evenly distributed over  $N = 3$  inverters

$$C_L/C_{g,1} = 8/1$$

$$f = \sqrt[3]{8} = 2$$

## Determining N: Optimal Number of Inverters


- What is the optimal value for N given F (=f<sup>N</sup>) ?
  - if the number of stages is too large, the intrinsic delay of the stages becomes dominate
  - if the number of stages is too small, the effective fan-out of each stage becomes dominate

- The optimum N is found by differentiating the minimum delay expression divided by the number of stages and setting the result to 0, giving

$$\gamma + \sqrt[N]{F} - (\sqrt[N]{F} \ln F)/N = 0$$





- For  $\gamma = 0$  (ignoring self-loading)  $N = \ln (F)$  and the effective-fan out becomes  $f = e = 2.71828$
- For  $\gamma = 1$  (the typical case) the optimum effective fan-out (tapering factor) turns out to be close to 3.6

# Optimum Effective Fan-Out

 

- ❑ Choosing  $f$  larger than optimum has little effect on delay and reduces the number of stages (and area).
  - Common practice to use  $f = 4$  (for  $\gamma = 1$ )
  - But **too many** stages has a substantial negative impact on delay

# Example of Inverter (Buffer) Staging
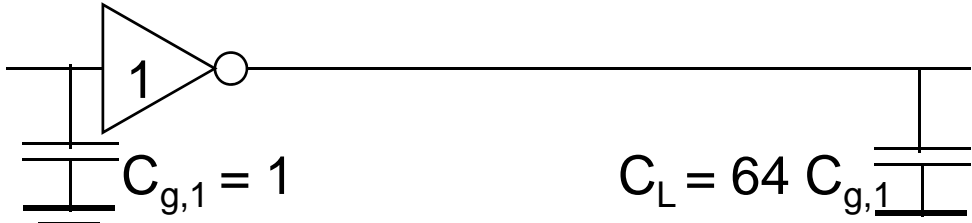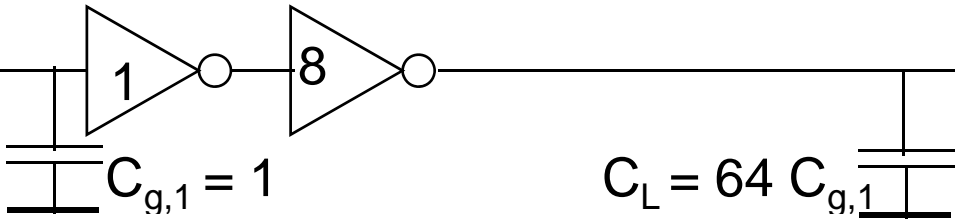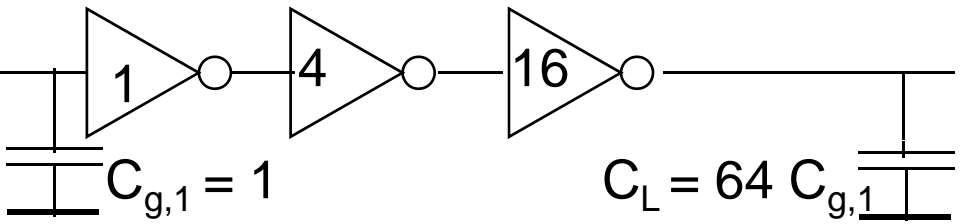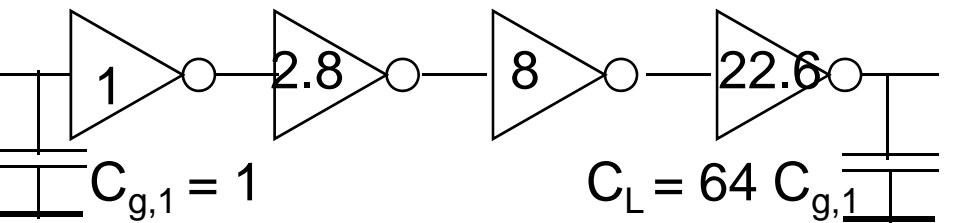
|  | N | f   | $t_p$ |
|--|---|-----|-------|
|  <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>   | 1 | 64  | 65    |
|  <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>   | 2 | 8   | 18    |
|  <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p>  | 3 | 4   | 15    |
|  <p> <math>C_{g,1} = 1</math> <math>C_L = 64 C_{g,1}</math> </p> | 4 | 2.8 | 15.3  |


## Impact of Buffer Staging for Large $C_L$

| <b>F (<math>\gamma = 1</math>)</b> | <b>Unbuffered</b> | <b>Two Stage Chain</b> | <b>Opt. Inverter Chain</b> |
|------------------------------------|-------------------|------------------------|----------------------------|
| 10                                 | 11                | 8.3                    | 8.3                        |
| 100                                | 101               | 22                     | 16.5                       |
| 1,000                              | 1001              | 65                     | 24.8                       |
| 10,000                             | 10,001            | 202                    | 33.1                       |

- ❑ Impressive speed-ups with optimized cascaded inverter chain for very large capacitive loads.
 
# Input Signal Rise/Fall Time

- ❑ In reality, the **input** signal changes gradually (and both PMOS and NMOS conduct for a brief time). This affects the current available for charging/discharging  $C_L$  and impacts propagation delay.
- ❑  $t_p$  increases **linearly** with increasing input slope,  $t_s$ , once  $t_s > t_p$
- ❑  $t_s$  is due to the limited driving capability of the preceding gate



for a minimum-size inverter  
with a fan-out of a single gate



## Design Challenge

---


- ❑ A gate is never designed in isolation: its performance is affected by both the fan-out and the driving strength of the gate(s) feeding its inputs.

$$t_p^i = t_{\text{step}}^i + \eta t_{\text{step}}^{i-1} \quad (\eta \approx 0.25)$$

- ❑ Keep signal rise times smaller than or equal to the gate propagation delays.
  - good for performance
  - good for power consumption
- ❑ Keeping rise and fall times of the signals small and of approximately equal values is one of the major challenges in high-performance designs - **slope engineering**.
 
## Delay with Long Interconnects

- When gates are farther apart, wire capacitance and resistance can no longer be ignored.



$$t_p = 0.69R_{dr}C_{int} + (0.69R_{dr} + 0.38R_w)C_w + 0.69(R_{dr} + R_w)C_{fan}$$

$$\text{where } R_{dr} = (R_{eqn} + R_{eqp})/2$$





$$= 0.69R_{dr}(C_{int} + C_{fan}) + 0.69(R_{dr}c_w + r_w C_{fan})L + 0.38r_w c_w L^2$$

- Wire delay rapidly becomes the dominate factor (due to the **quadratic term**) in the delay budget for longer wires.


---

# Rabaey 5.4.2

# Switch Delay Model

    


# Input Pattern Effects on Delay

 

- ❑ Delay is dependent on the **pattern** of inputs
- ❑ Low to high transition
  - both inputs go low
    - delay is  $0.69 R_p/2 C_L$  since two p-resistors are on in parallel
  - one input goes low
    - delay is  $0.69 R_p C_L$
- ❑ High to low transition
  - both inputs go high
    - delay is  $0.69 2R_n C_L$
- ❑ Adding transistors in series (without sizing) slows down the circuit


 
# Delay Dependence on Input Patterns

2-input NAND with  
 NMOS =  $0.5\mu\text{m}/0.25\mu\text{m}$   
 PMOS =  $0.75\mu\text{m}/0.25\mu\text{m}$   
 $C_L = 10\text{ fF}$




| Input Data Pattern | Delay (psec) |
|--------------------|--------------|
| A=B=0→1            | 69           |
| A=1, B=0→1         | 62           |
| A= 0→1, B=1        | 50           |
| A=B=1→0            | <b>35</b>    |
| A=1, B=1→0         | <b>76</b>    |
| A= 1→0, B=1        | 57           |

# Transistor Sizing

  


# Transistor Sizing a Complex CMOS Gate

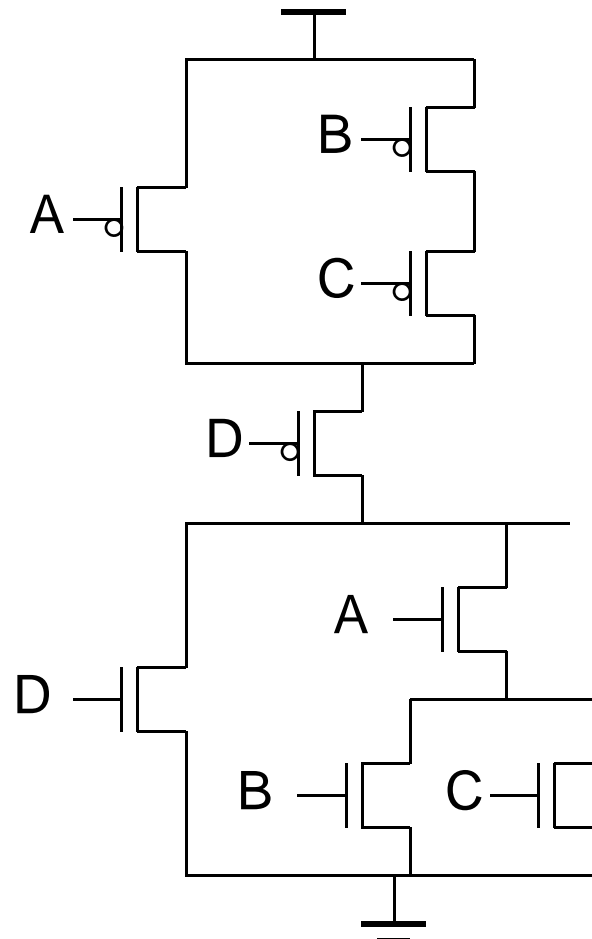

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$





# Transistor Sizing a Complex CMOS Gate

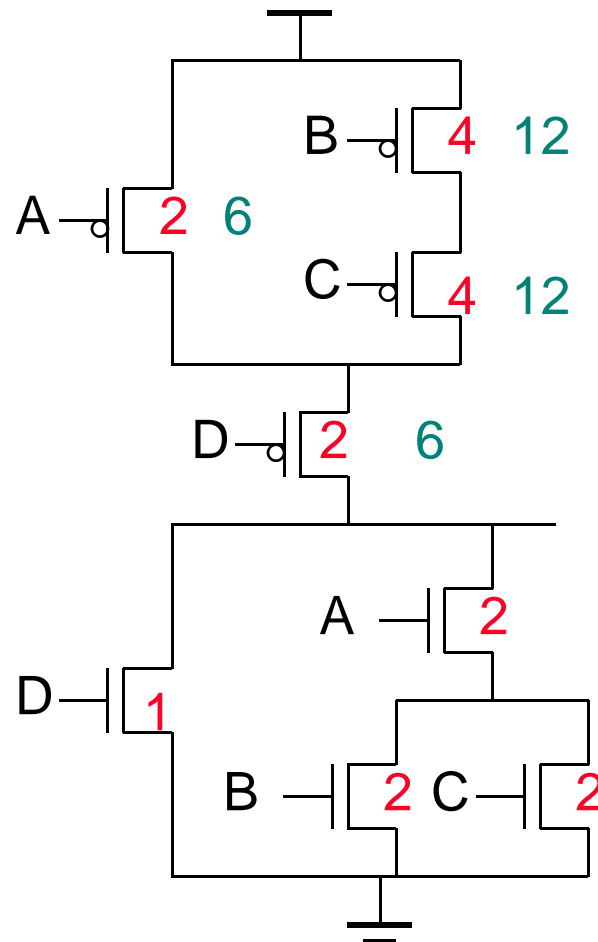

$$\text{OUT} = \neg(D + A \cdot (B + C))$$

# Fan-In Considerations

 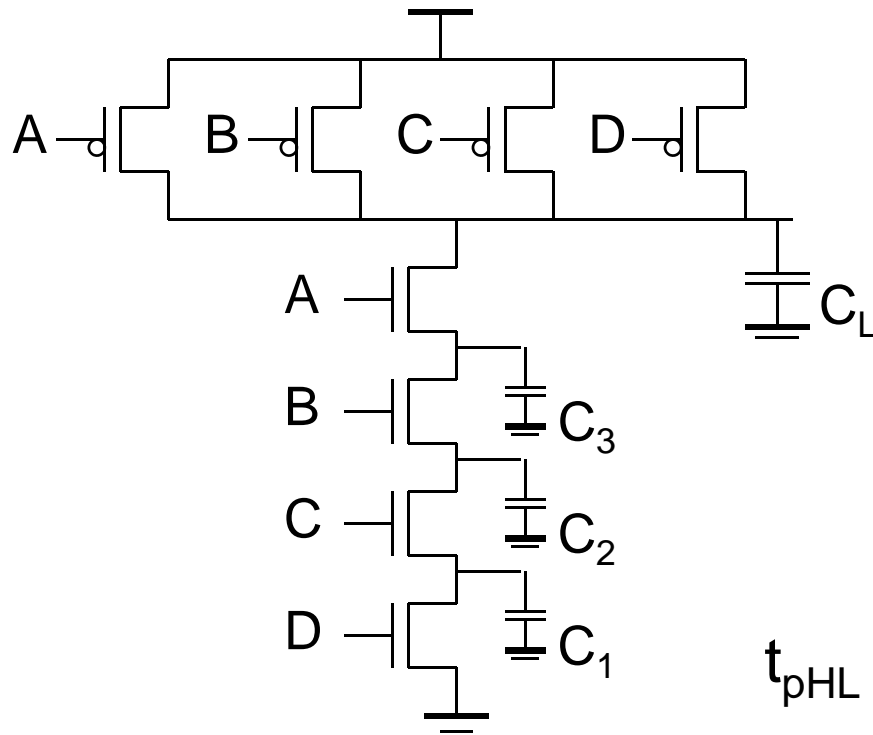


Distributed RC model  
(Elmore delay)

$$t_{pHL} = 0.69 R_{eqn} (C_1 + 2C_2 + 3C_3 + 4C_L)$$

Propagation delay deteriorates rapidly as a function of fan-in – **quadratically** in the worst case.

# $t_p$ as a Function of Fan-In

 


□ Gates with a fan-in greater than 4 should be avoided.

# Fast Complex Gates: Design Technique 1

- ❑ Transistor sizing
  - as long as fan-out capacitance dominates

- ❑ Progressive sizing

 

Distributed RC line

$$M1 > M2 > M3 > \dots > MN$$



(the fet closest to the **output** should be the smallest)

Can reduce delay by more than 20%; decreasing gains as technology shrinks

# Fast Complex Gates: Design Technique 2
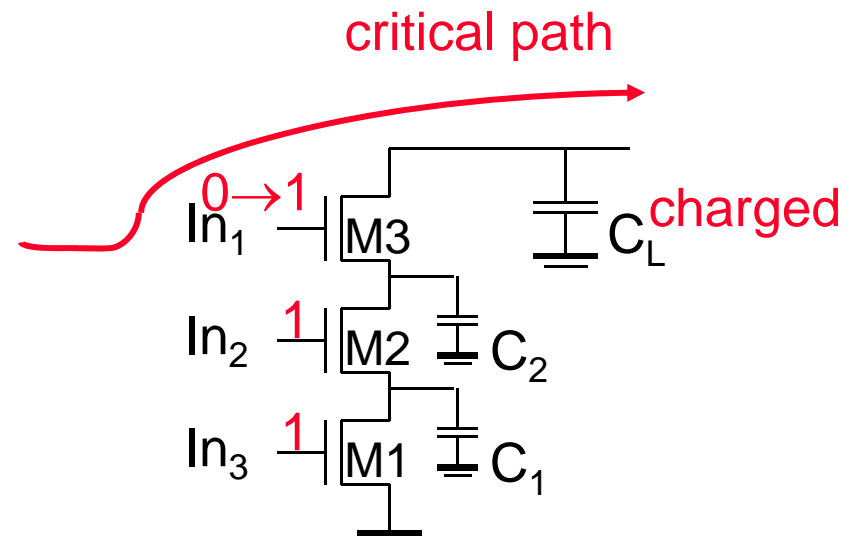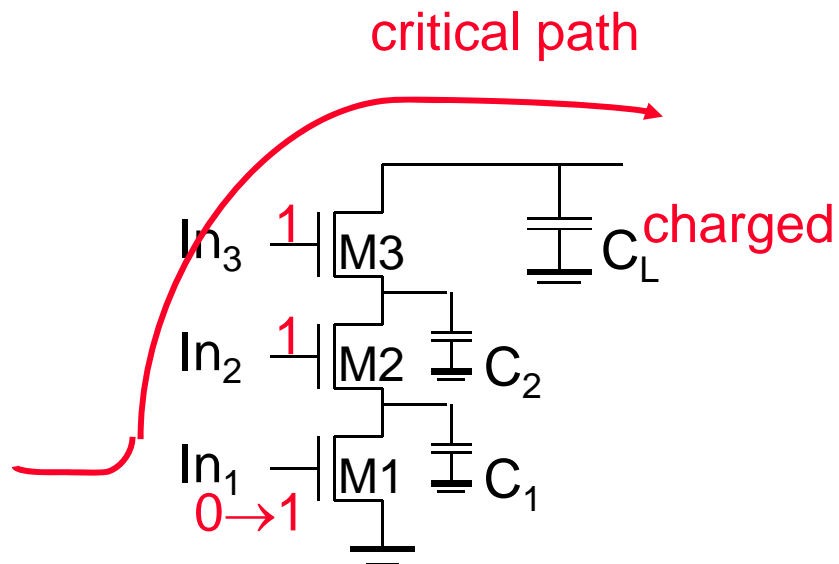
## □ Input re-ordering


- when not all inputs arrive at the same time




# Fast Complex Gates: Design Technique 2
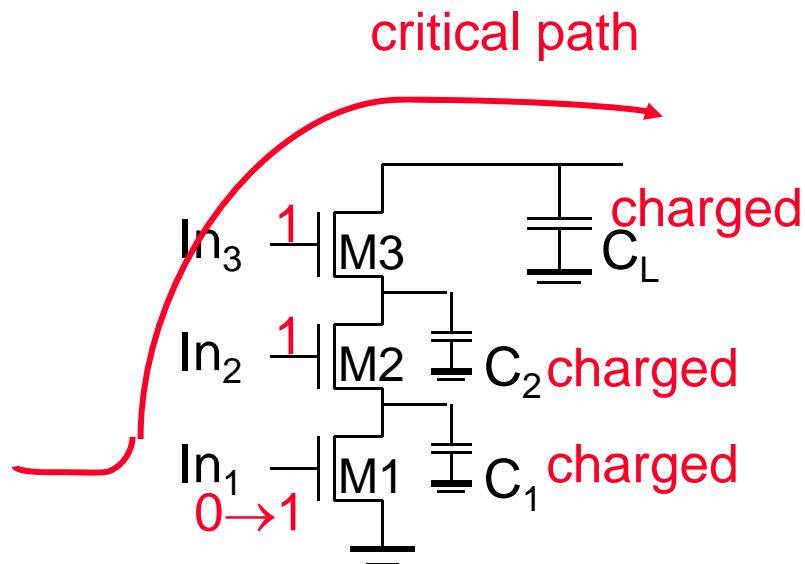
## □ Input re-ordering

- when not all inputs arrive at the same time





 delay determined by time to discharge  $C_L$ ,  $C_1$  and  $C_2$



delay determined by time to discharge  $C_L$

# Sizing and Ordering Effects

 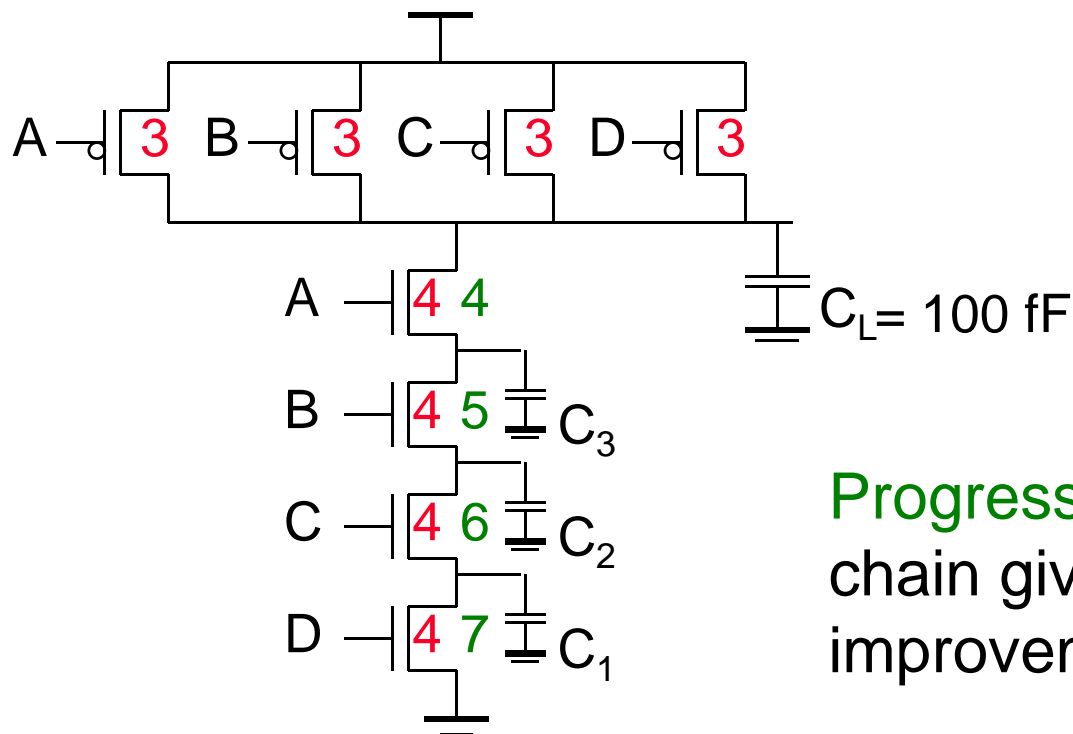


Progressive sizing in pull-down chain gives up to a 23% improvement.

Input ordering saves 5%  
critical path A – 23%  
critical path D – 17%

# Fast Complex Gates: Design Technique 3

- Alternative logic structures


$$F = ABCDEFGH$$

 


 
## Fast Complex Gates: Design Technique 4

- ❑ Isolating fan-in from fan-out using buffer insertion



- ❑ Real lesson is that optimizing the propagation delay of a gate in isolation is misguided.

## Fast Networks: Design Technique 5 - Logical Effort

- The optimum fan-out for a chain of N inverters driving a load  $C_L$  is

$$f = \sqrt[N]{C_L/C_{in}}$$

- so, if we can, keep the fan-out per stage around 4.
- Can the same approach (**logical effort**) be used for any combinational circuit?

- For a complex gate, we expand the inverter equation

$$t_p = t_{p0} (1 + C_{ext}/\gamma C_g) = t_{p0} (1 + f/\gamma)$$

to

$$t_p = t_{p0} (p + g f/\gamma)$$

- $t_{p0}$  is the intrinsic delay of an inverter
- $f$  is the effective fan-out ( $C_{ext}/C_g$ ) – also called the **electrical effort**
- $p$  is the ratio of the intrinsic (unloaded) delay of the complex gate and a simple inverter (a function of the gate topology and layout style)
- $g$  is the **logical effort**