

Introduction to CMOS VLSI Design

Lecture 6: Wires

Outline


- ☐ Introduction
- ☐ Wire Resistance
- ☐ Wire Capacitance
- ☐ Wire RC Delay
- ☐ Crosstalk
- ☐ Wire Engineering
- ☐ Repeaters

Introduction

- ❑ Chips are mostly made of wires called *interconnect*
 - In stick diagram, wires set size
 - Transistors are little things under the wires
 - Many layers of wires
- ❑ Wires are as important as transistors
 - Speed
 - Power
 - Noise
- ❑ Alternating layers run orthogonally

Wire Geometry

 - ❑ Pitch = $w + s$
- ❑ Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires




Layer Stack

- ❑ AMI 0.6 μm process has 3 metal layers
- ❑ Modern processes use 6-10+ metal layers
- ❑ Example:

Intel 180 nm process

- ❑ M1: thin, narrow ($< 3\lambda$)
 - High density cells
- ❑ M2-M4: thicker
 - For longer wires
- ❑ M5-M6: thickest
 - For V_{DD} , GND, clk


Layer	T (nm)	W (nm)	S (nm)	AR
6	1720	860	860	2.0
	1000			
5	1600	800	800	2.0
	1000			
4	1080	540	540	2.0
	700			
3	700	320	320	2.2
	700			
2	700	320	320	2.2
	700			
1	480	250	250	1.9
	800			

 

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$


$R =$

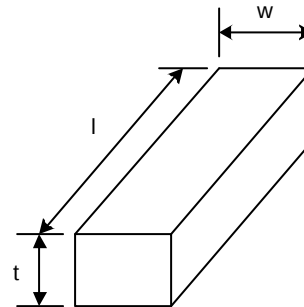

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$

$$R = \frac{\rho}{t} \frac{l}{w}$$

 

Wire Resistance


□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$

$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

□ $R_{\square} = \text{sheet resistance } (\Omega/\square)$
– □ is a dimensionless unit(!)

□ Count number of squares
– $R = R_{\square} * (\# \text{ of squares})$

Identical Resistance

 

Choice of Metals

- ❑ Until 180 nm generation, most wires were aluminum
- ❑ Modern processes often use copper
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

Metal	Bulk resistivity ($\mu\Omega\cdot\text{cm}$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Molybdenum (Mo)	5.3

Sheet Resistance

- Typical sheet resistances in 180 nm process

Layer	Sheet Resistance ($\Omega/\square$)
Diffusion (silicided)	3-10
Diffusion (no silicide)	50-200
Polysilicon (silicided)	3-10
Polysilicon (no silicide)	50-400
Metal1	0.08
Metal2	0.05
Metal3	0.05
Metal4	0.03
Metal5	0.02
Metal6	0.02


Contacts Resistance

- ❑ Contacts and vias also have 2-20 Ω
- ❑ Use many contacts for lower R
 - Many small contacts for current crowding around periphery



Wire Capacitance (R&C결합)

 - ❑ Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- ❑ $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$




Capacitance Trends

- ❑ Parallel plate equation: $C = \epsilon A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (W, t) increases capacitance
 - Increasing distance (s, h) decreases capacitance
- ❑ Dielectric constant
 - $\epsilon = k\epsilon_0$
- ❑ $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm
- ❑ $k = 3.9$ for SiO_2
- ❑ Processes are starting to use low-k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

M2 Capacitance Data

 - Typical wires have $\sim 0.2 \text{ fF}/\mu\text{m}$
 - Compare to $2 \text{ fF}/\mu\text{m}$ for gate capacitance




Diffusion & Polysilicon

- ❑ Diffusion capacitance is very high (about 2 fF/ μm)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion *runners* for wires!
- ❑ Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Lumped Element Models

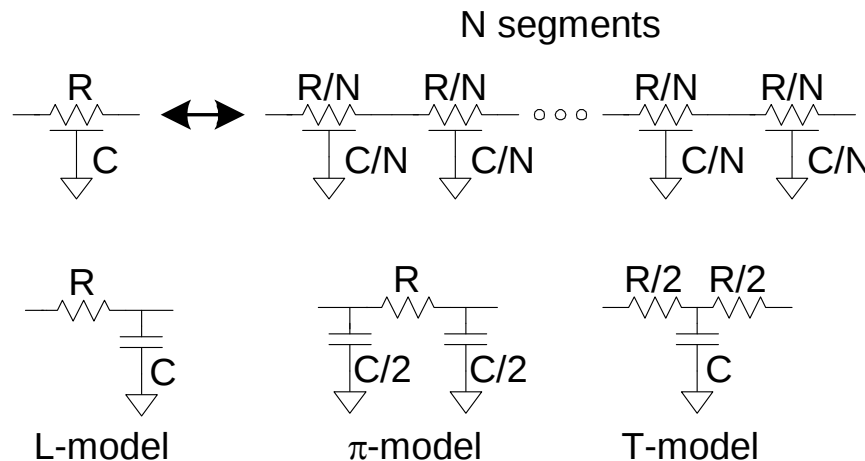- ❑ Wires are a distributed system
 - Approximate with lumped element models




- ❑ 3-segment π -model is accurate to 3% in simulation
- ❑ L-model needs 100 segments for same accuracy!
- ❑ Use single segment π -model for Elmore delay

Example

- ❑ Metal2 wire in 180 nm process
 - 5 mm long
 - 0.32 μm wide
- ❑ Construct a 3-segment π -model
 - $R_{\square} =$
 - $C_{\text{permicron}} =$

 Example

- ❑ Metal2 wire in 180 nm process
 - 5 mm long
 - 0.32 μm wide
- ❑ Construct a 3-segment π -model 5mm/0.32um*sheet R
 - $R_{\square} = 0.05 \Omega/\square$ $\Rightarrow R = 781 \Omega$
 - $C_{\text{permicron}} = 0.2 \text{ fF}/\mu\text{m}$ *5mm $\Rightarrow C = 1 \text{ pF}$



Wire RC Delay


- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example.
 - $R = 2.5 \text{ k}\Omega \cdot \mu\text{m}$ for gates
 - Unit inverter: $0.36 \mu\text{m}$ nMOS, $0.72 \mu\text{m}$ pMOS

– $t_{pd} =$

Wire RC Delay

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example.

 - $R = 2.5 \text{ k}\Omega/\mu\text{m}$ for gates (10X gate)
- Unit inverter: $0.36 \mu\text{m}$ nMOS, $0.72 \mu\text{m}$ pMOS




Crosstalk

- ❑ A capacitor does not like to change its voltage instantaneously.
- ❑ A wire has high capacitance to its neighbor.
 - When the neighbor switches from 1- $\rightarrow$ 0 or 0- $\rightarrow$ 1, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*.
- ❑ Crosstalk effects
 - Noise on nonswitching wires
 - Increased delay on switching wires

Crosstalk Delay

 
- ❑ Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- ❑ Effective C_{adj} depends on behavior of neighbors
 - *Miller effect*



B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant			
Switching with A			
Switching opposite A			

Crosstalk Delay

 - ❑ Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$ (Because above & below @ const. V) Small signal GND in case of Vdd
- ❑ Effective C_{adj} depends on behavior of neighbors
 - *Miller effect*(remember 전자회로, think of effective terminal vtg.)




B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant	V_{DD}	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	C_{gnd}	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2 C_{\text{adj}}$	2

Crosstalk Noise

- ❑ Crosstalk causes noise on nonswitching wires
- ❑ If victim is floating:
 - model as capacitive voltage divider
 
$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor} \quad 1/C_g / (1/C_g + 1/C_a)$$



Driven Victims (w/o derivation)

- Usually victim is driven by a ^(not floating as previous slide) _(logic) gate that fights noise
 - Noise depends on relative resistances ^{Aggressor dominates & victim in intermediate range}
 - Victim driver is in linear region, agg. in saturation
 - If sizes are same, $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \left[\frac{1}{1+k} \Delta V_{\text{aggressor}} \right]$$

Vaggressor to Vx factor
(Detailed derivation, refer to ref. paper)

Vx to Vvictim factor
(as in the previous slide)

If C is equal, $1/2 * (1 + R_a/R_v)$
Smaller the victim gate (larger R_v),
Larger the damage

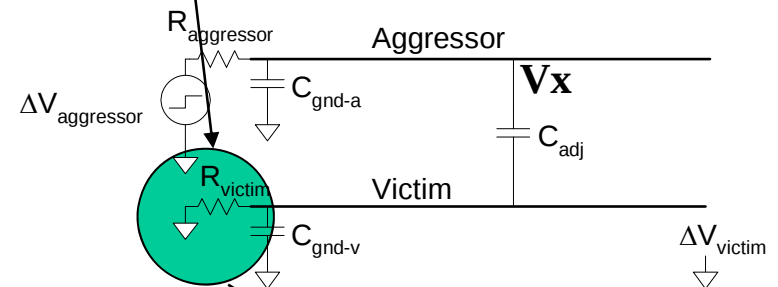
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$



Instead of floating victim,
gate driven victim (noise reduced)

Coupling Waveforms

 - Simulated coupling for $C_{adj} = C_{victim}$



Noise Implications



- ❑ *So what* if we have noise?
- ❑ If the noise is less than the noise margin, nothing happens
- ❑ Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- ❑ Dynamic logic never recovers from glitches
- ❑ Memories and other sensitive circuits also can produce the wrong answer

Wire Engineering

- ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:

Wire Engineering

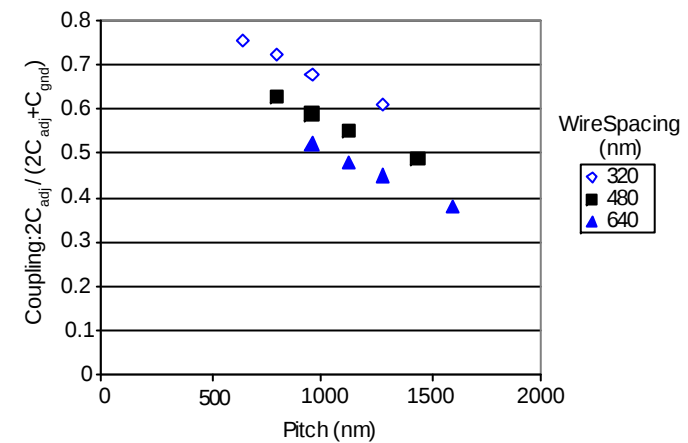
 
- ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:
 - Width
 - Spacing



Larger the width, smaller the delay,
Larger the spacing, smaller the coupling

Wire Engineering

  - ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:
 - Width
 - Spacing
 - Layer






Wire Engineering

- ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:

- Width
- Spacing
- Layer
- Shielding

   Shield noise sensitive wires
with power lines





Repeaters

- ❑ R and C are proportional to l
- ❑ RC delay is proportional to l^2
 - Unacceptably great for long wires

Repeaters

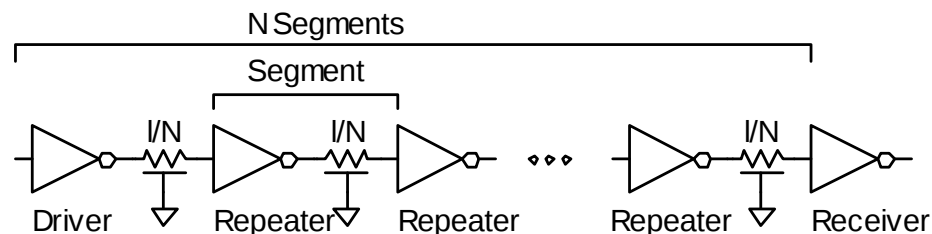 - ❑ R and C are proportional to l
- ❑ RC delay is proportional to l^2
 - Unacceptably great for long wires
- ❑ Break long wires into N shorter segments
 - Drive each one with an inverter or buffer




Repeater Design

- ❑ How many repeaters should we use?
- ❑ How large should each one be?
- ❑ Equivalent Circuit
 - Wire length l/N (*total length l divided by N sections*)
 - Wire Capacitance $C_w * l/N$, Resistance $R_w * l/N$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W

Repeater Design

 - ❑ How many repeaters should we use?
 - ❑ How large should each one be?
 - ❑ Equivalent Circuit
 - Wire length l
 - Wire Capacitance $C_w * l$, Resistance $R_w * l$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W
- All quantity per unit length*
- $C' \rightarrow 3C(C_{ox}) \text{ 2W PMOS 1W NMOS}$



Repeater Results

(Derivation @next slide)

- Write equation for Elmore Delay
 - Differentiate with respect to W and N
 - Set equal to 0, solve

$$\frac{l}{N} = \sqrt{\frac{2RC'}{R_w C_w}}$$

$$\frac{t_{pd}}{l} = (2 + \sqrt{2}) \sqrt{RC' R_w C_w}$$

$$W = \sqrt{\frac{RC_w}{R_w C'}}$$

Best delay that can be
minimized (optimized)
per length

~60-80 ps/mm

in 180 nm process

Derivation

The Elmore delay of each segment is Slide 35의 Schematic 기준

$$t_{pd-seg} = \frac{R}{W} \left(\frac{C_w l}{N} + C' W \right) + \left(\frac{R_w l}{N} \right) \left(\frac{C_w l}{2N} + C' W \right)$$

The total delay is N times greater:

$$t_{pd} = NRC' + L \left(R_w C' W + \frac{RC_w}{W} \right) + L^2 \frac{R_w C_w}{2N}$$

Take the partial derivatives with respect to N and W and set them to 0 to minimize delay:

$$\begin{aligned} \frac{\partial t_{pd}}{\partial N} &= RC' - l^2 \frac{R_w C_w}{2N^2} = 0 \Rightarrow N = l \sqrt{\frac{R_w C_w}{2RC'}} \\ \frac{\partial t_{pd}}{\partial W} &= l \left(R_w C' - \frac{RC_w}{W^2} \right) = 0 \Rightarrow W = \sqrt{\frac{RC_w}{R_w C'}} \end{aligned}$$

Using these gives a delay per unit length of

$$\frac{t_{pd}}{l} = (2 + \sqrt{2}) \sqrt{RC' R_w C_w}$$